

1A.

!S	!R	Q _{curr}	Q _{new}
0	0	0	undefined
0	0	1	Undefined
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

latch operation			
S'	R'	Action	
0	0	not allowed	
0	1	Q = 1	
1	0	Q = 0	
1	1	No Change	

1B.

This is an alternate model of the simple SR latch which is built with NAND logic gates. Set and reset now become active low signals, denoted S' and R' respectively. Otherwise, operation is identical to that of the SR latch.


2.

Solution:

Current State		Input X	Next State	
A	B		A	B
0	0	0	1	0
0	0	1	0	0
0	1	0	1	0
0	1	1	0	0
1	0	0	0	0
1	0	1	0	0
1	1	0	0	1
1	1	1	0	1

3.

Solution:

 

4. A. $256 \text{ MB} = 2^8 * 2^{20} \text{ Bytes} = 2^{28} \text{ Bytes}$. Hence 28 bits needed for addressing.

B. 34 bits can address 2^{34} Bytes . $2^{34} = 2^{30} * 2^4 = 16 \text{ GB}$.

C. 34 bits can address 2^{34} words. As each word is 64 bits (8 Bytes), 34 bits can address $2^{34} * 8 \text{ Bytes} = 2^{30} * 2^4 * 2^3 \text{ B} = 128 \text{ GB}$

D. $256 \text{ MB} = 2^{28} \text{ Bytes}$. Number of bytes per word = 8 (2^3). Therefore, number of words in $256 \text{ MB} = 2^{28} / 2^3 = 2^{25}$. 25 bits are needed to address 2^{25} words.

5.

Solution:

A	B	C	O/P
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

