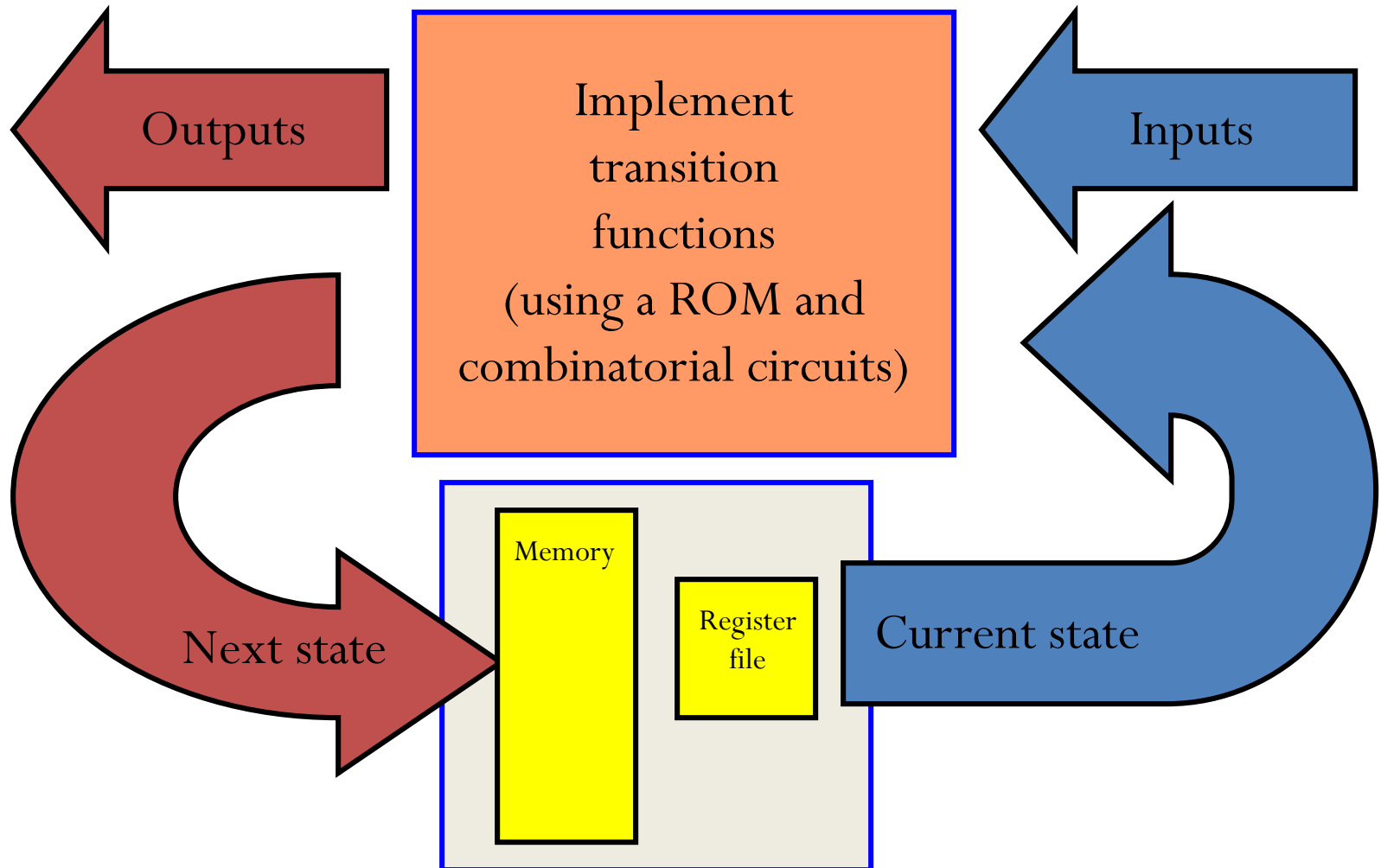


Microarchitecture


Outline

- **Introduction to Microarchitecture**
- ANNA Datapath
- ANNA Control
- Performance
- Pipelining
- Additional Performance Optimizations


Processor as a FSM



Microarchitecture Building Blocks

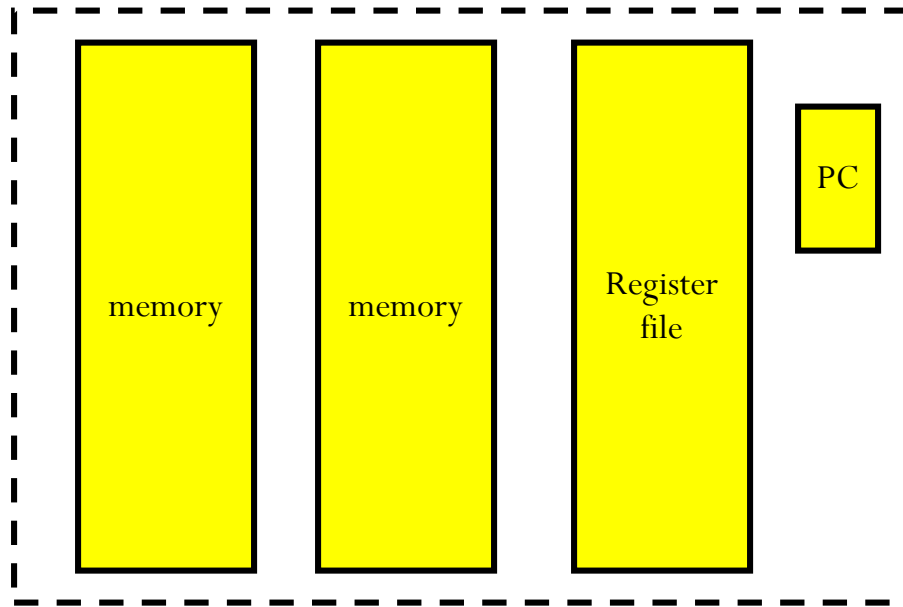


State

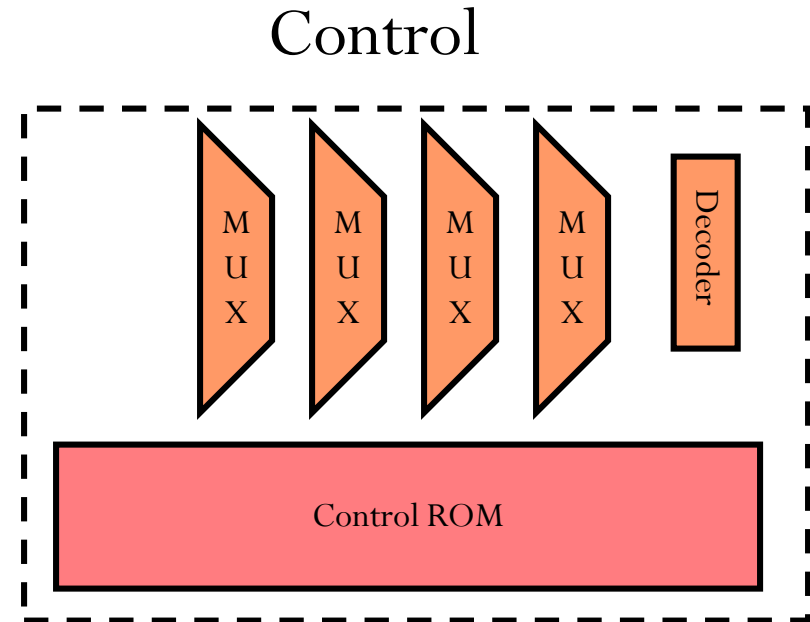

Control

Compute

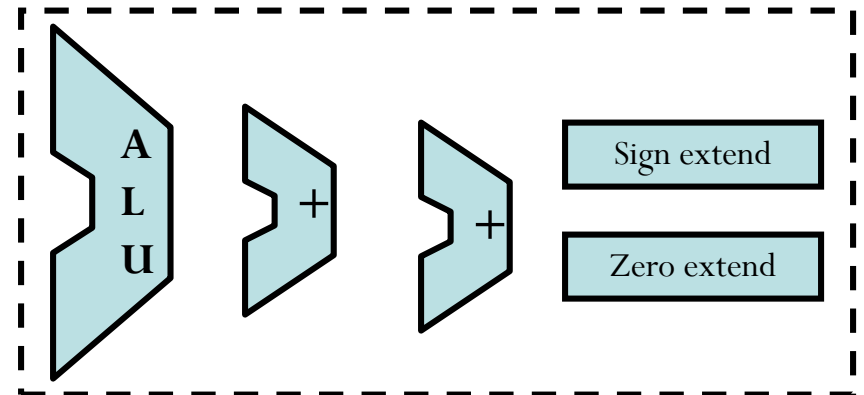

Datapath and Control

Common to decomposes the system in two parts:

- **Datapath:** A collection of interconnected modules that perform all the relevant computation on the data.
 - For a CPU: Set of components that perform arithmetic operations and hold data.
- **Control Unit:** Coordinates the behavior of the datapath by issuing appropriate control signals.
 - For a CPU: Commands the datapath, memory, I/O devices, according to the current instruction.


Outline

- Introduction to Microarchitecture
- **ANNA Datapath**
- ANNA Control
- Performance
- Pipelining
- Additional Performance Optimizations

ANNA Datapath Assumptions

- Datapath will omit these instructions:
 - `jalr`: left as an exercise
 - `in, out`: requires special I/O hardware
- Ignore startup: assume registers, memory, and PC have proper initial state.
- Initial datapath will be single cycle. Each instruction takes one cycle to execute.



ALU

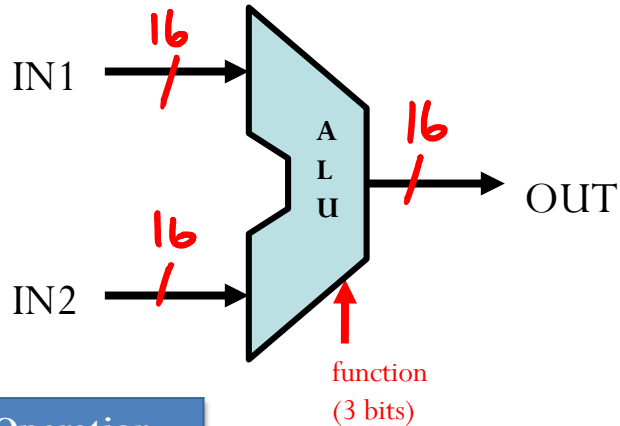

- For instructions listed, function bits are the lower three bits of the opcode.
 - `addi` also uses `add`
- For `lui` instructions:
 - IN1 contains current value of Rd (for lower 8 bits)
 - IN2 contains immediate
- For `lli` instructions:
 - IN1 is ignored
 - IN2 contains immediate.

Function	Operation
000	add
001	sub
010	and
011	or
100	not
101	shf
110	lli
111	lui


Compute Building Blocks

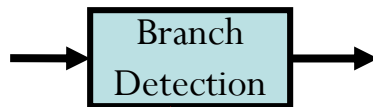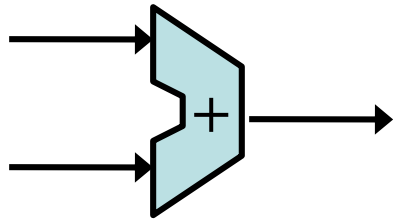

↑
branch type
(2 bits)


- Adder only adds numbers.
- Sign extension converts smaller number into 16-bit number by extending sign.
- Branch detection determines if a branch should be taken or not.
 - branch type input:
 - 00: bez
 - 01: bgz
 - 11: no branch
 - output:
 - 1: branch taken
 - 0: branch not taken

Register File

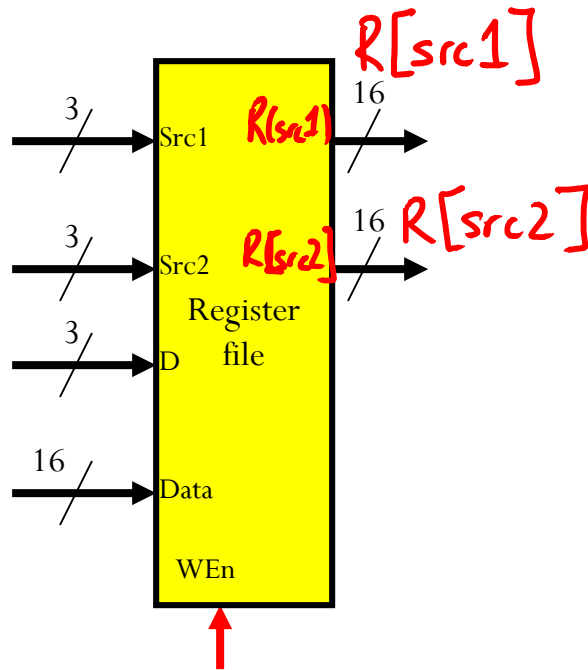


- Contains 8 registers.
 - Each is 16 bits.
- Two read ports (Src1, Src2) and one write (D) port.
 - Contains register number.
- Always enabled – can always read data.
- Write enable signal will be set for instructions that write to the register file.
- Has special logic to ignore writes to register 0.


Memory

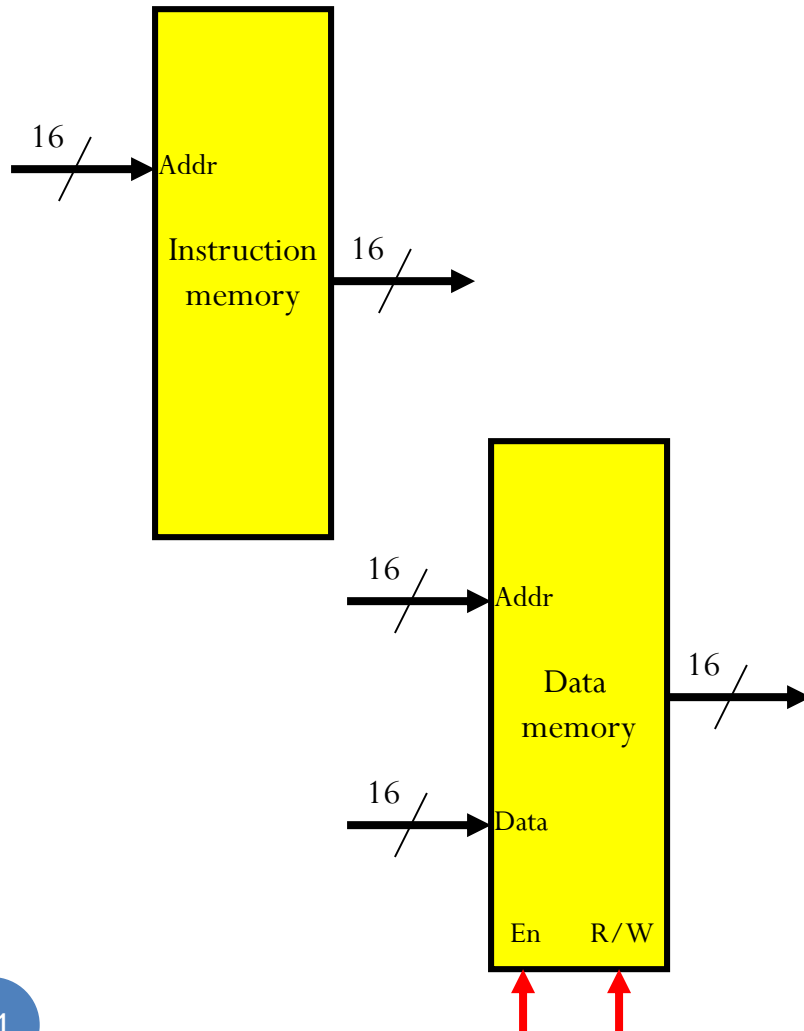

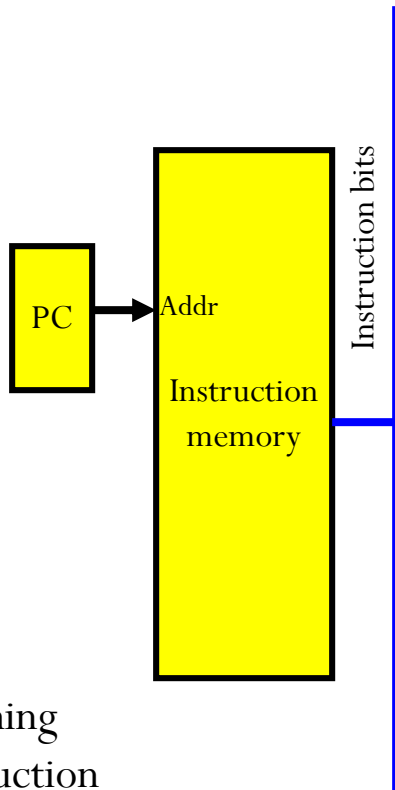- Two separate memories
 - one for instructions
 - one for data
- Will be replaced with caches later
 - instruction and data caches are separate
- Ignore case where code uses value written to data memory
 - no self-modifying code
- Instruction memory is always enabled and can only read.
- Data memory has an enable (En) signal (set for `lw/sw`) and R/W signal (read: 0, write: 1).




Fetching
instruction
from
memory.

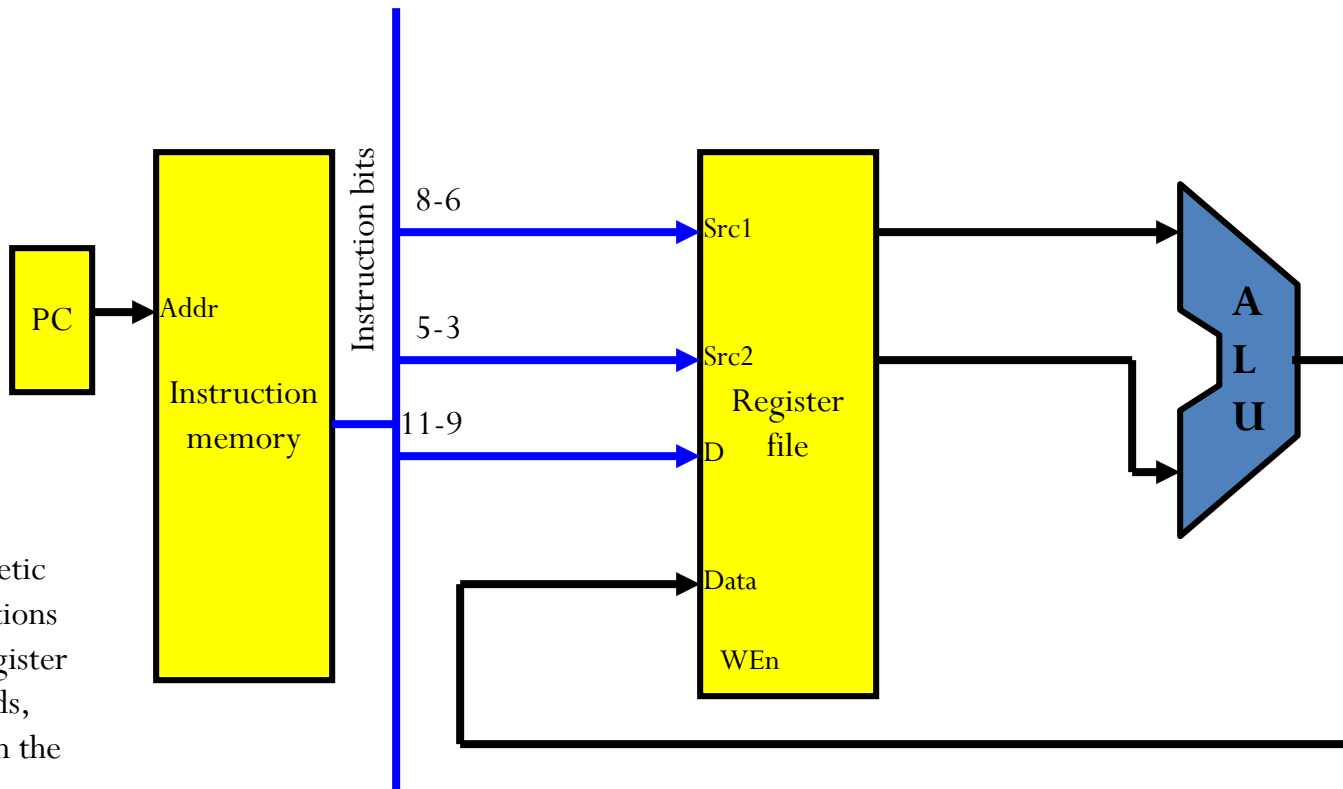


Arithmetic instructions read register operands, perform the desired operation in the ALU, and write back to register.

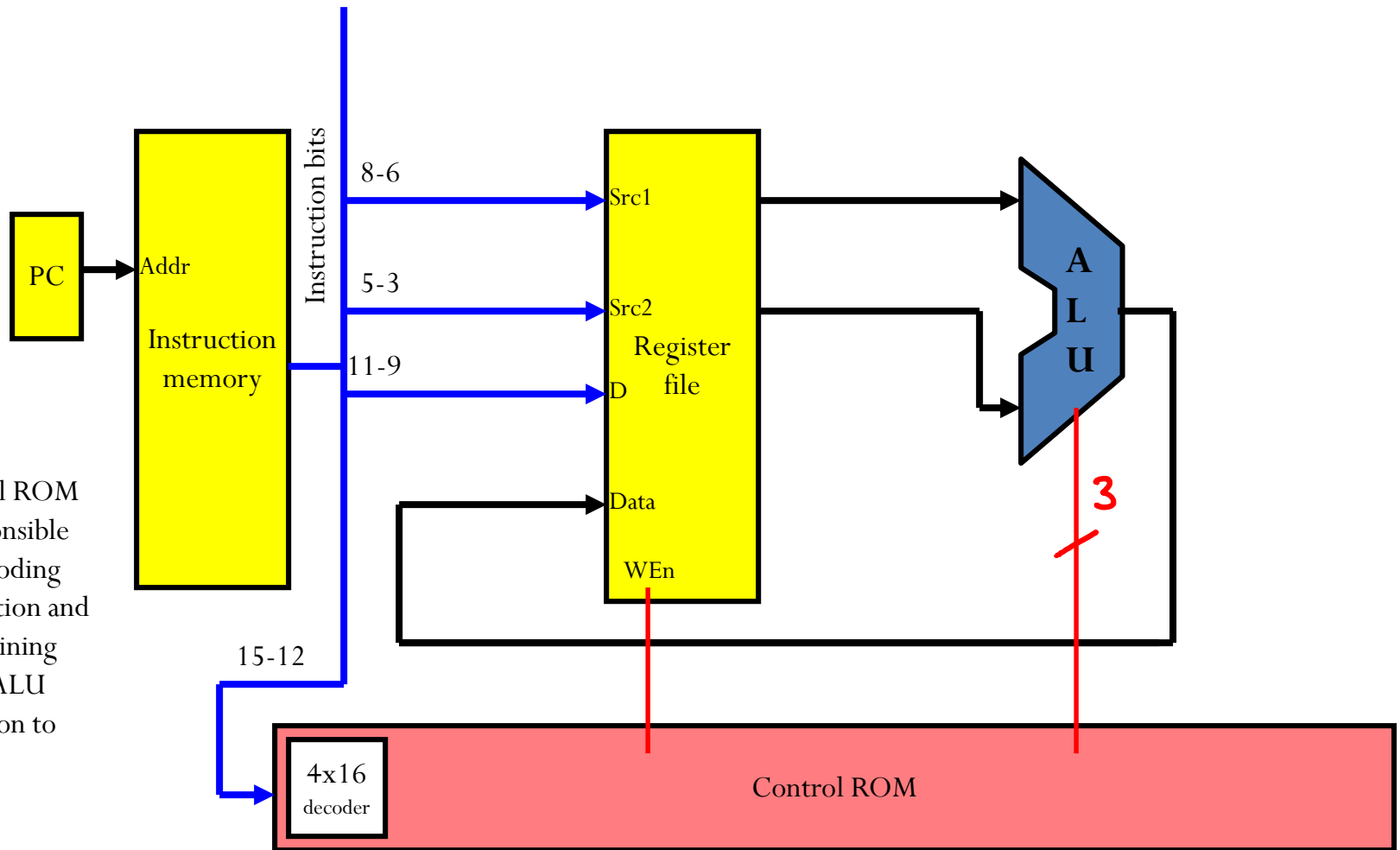
Control ROM is responsible for decoding instruction and determining which ALU operation to use.




Need to
increment PC.

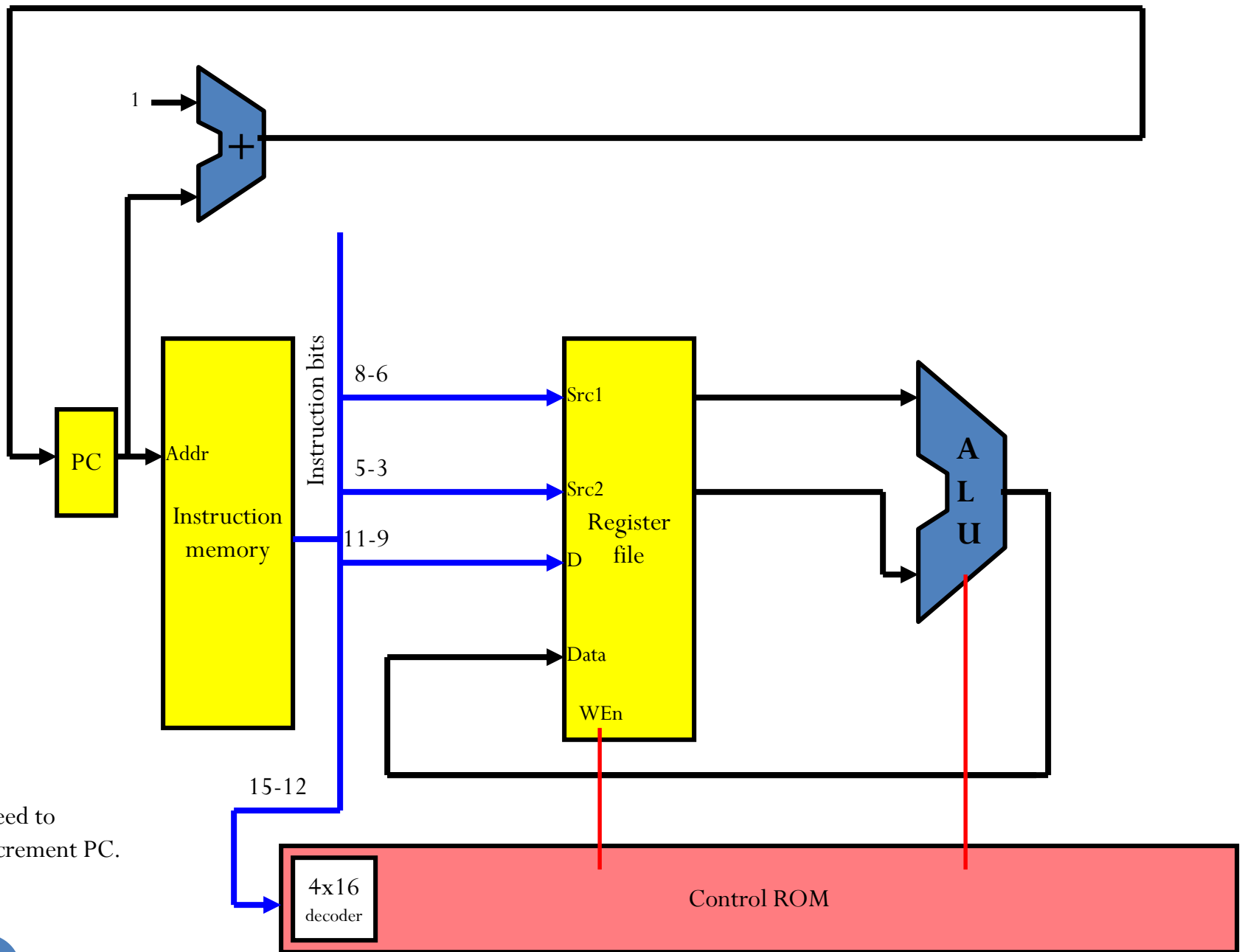


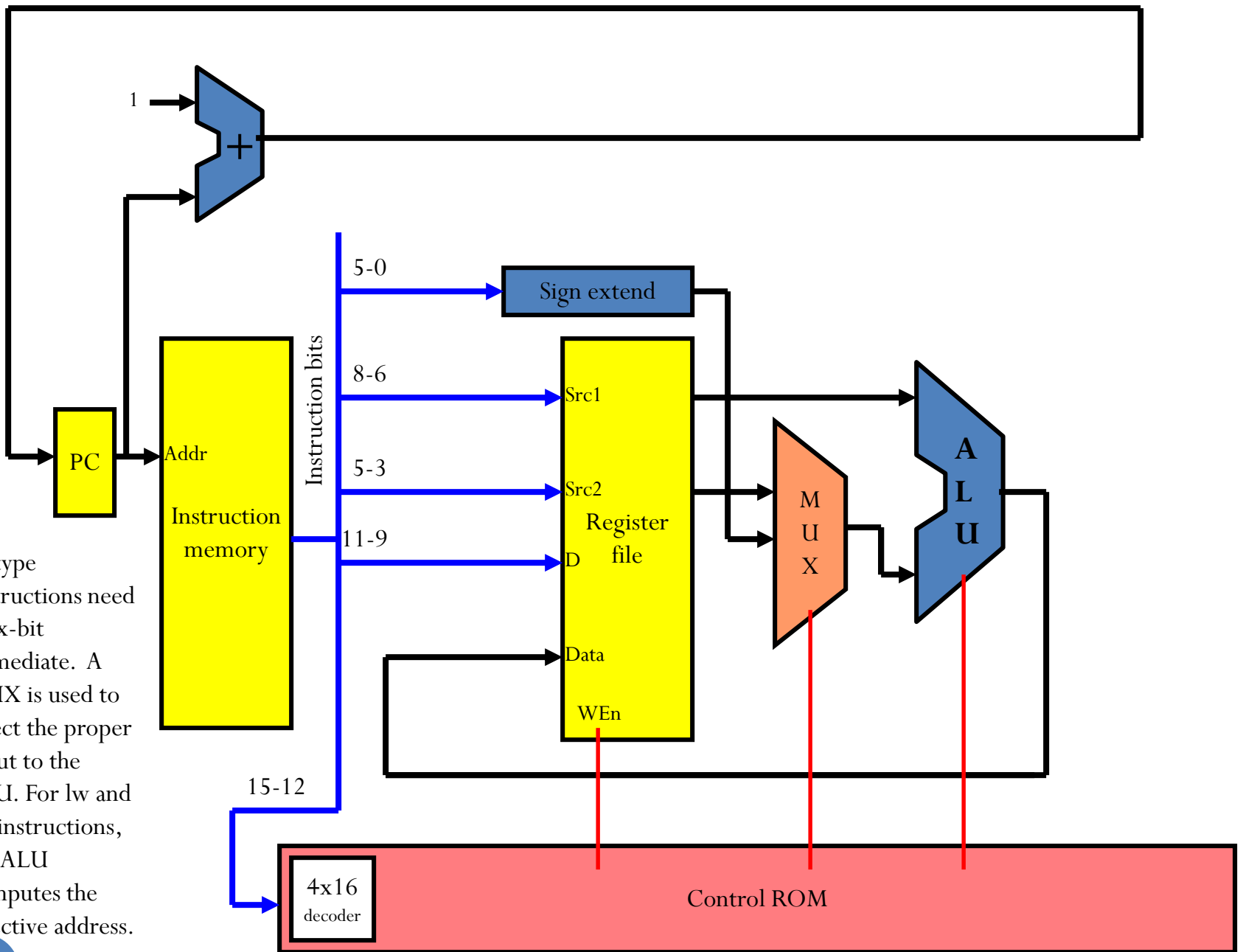I6-type instructions need a six-bit immediate. A MUX is used to select the proper input to the ALU. For lw and sw instructions, the ALU computes the effective address.




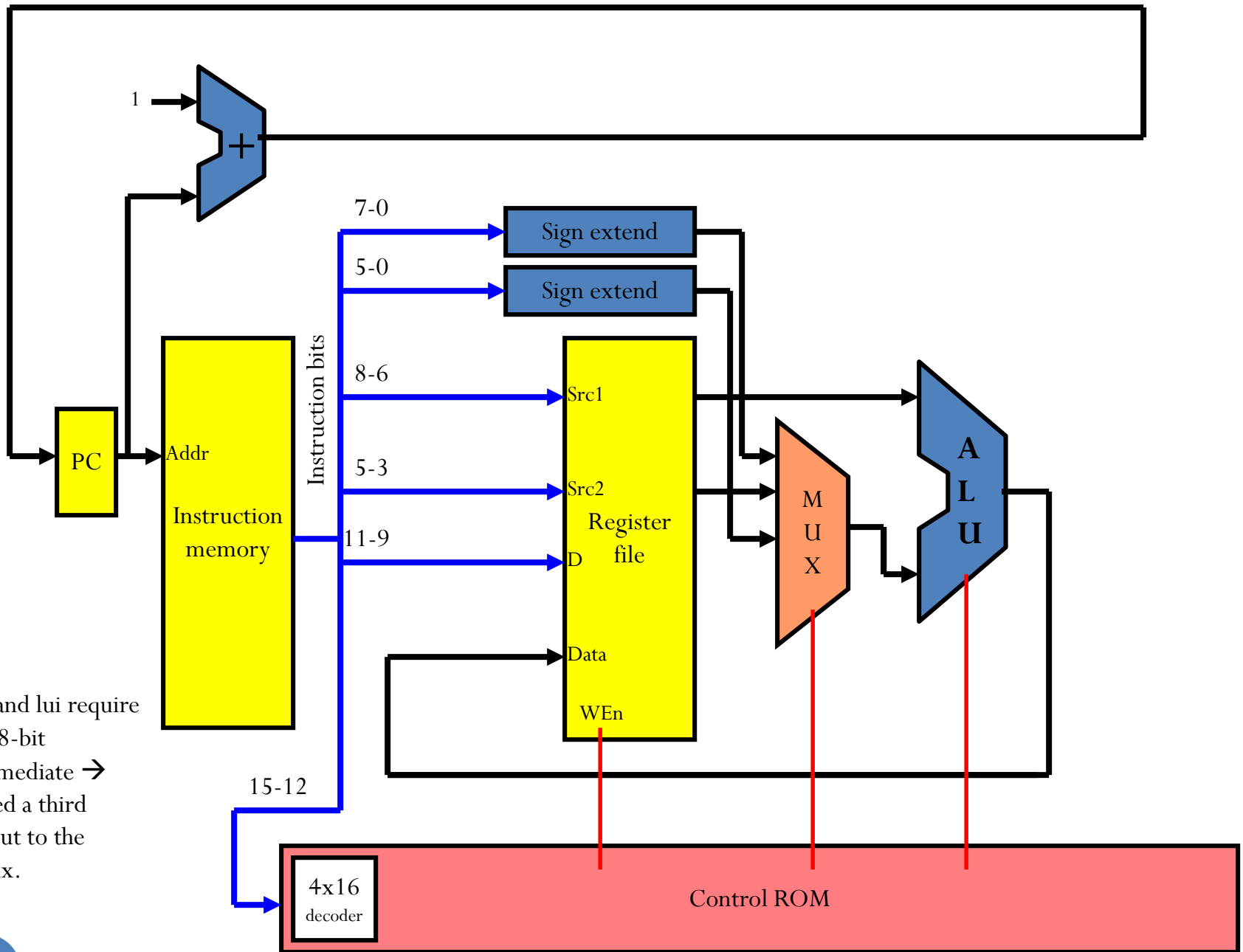lli and lui require
an 8-bit
immediate →
need a third
input to the
mux.




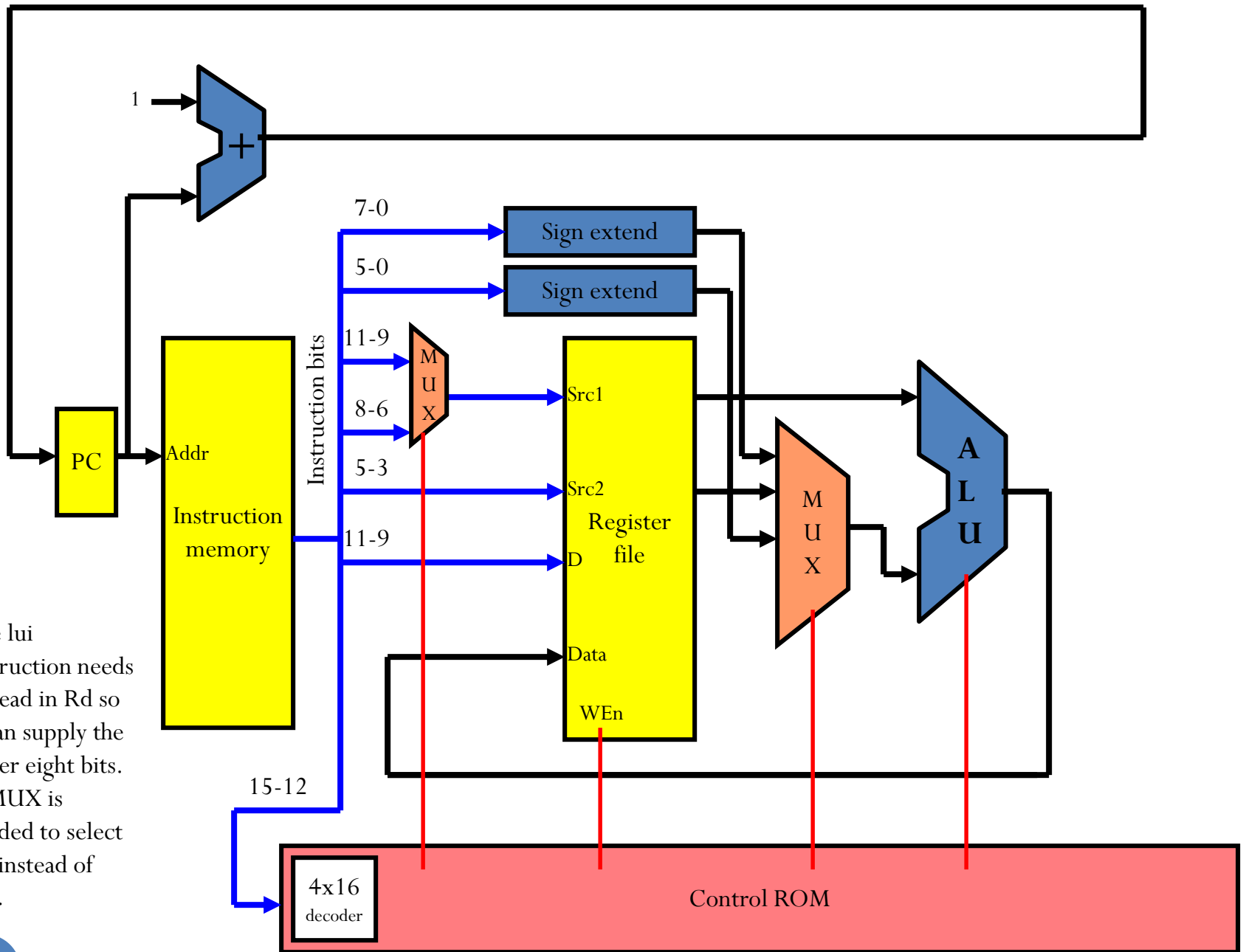

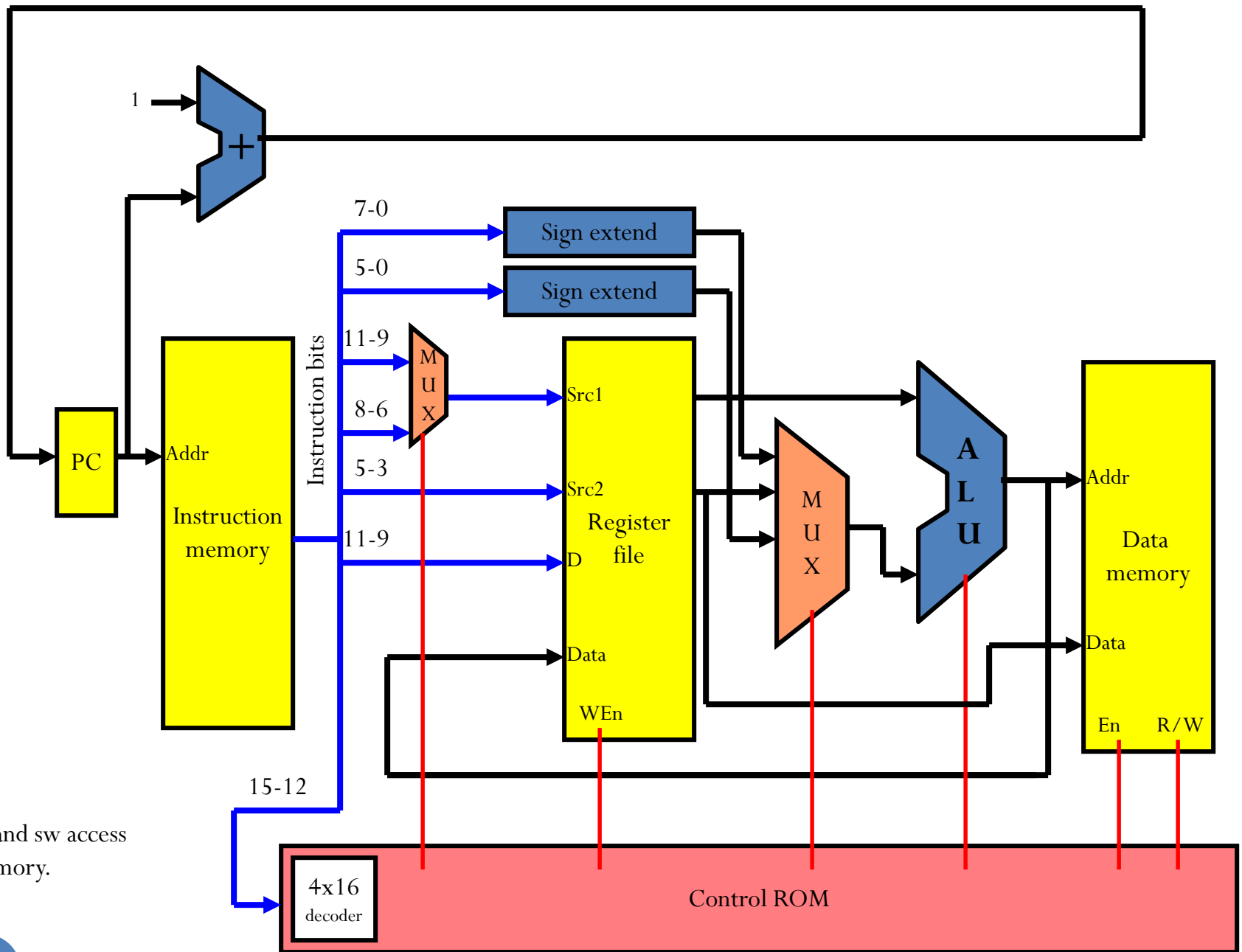
The `lui` instruction needs to read in `Rd` so it can supply the lower eight bits. A MUX is needed to select `Rd` instead of `Rs1`.




lw and sw access
memory.

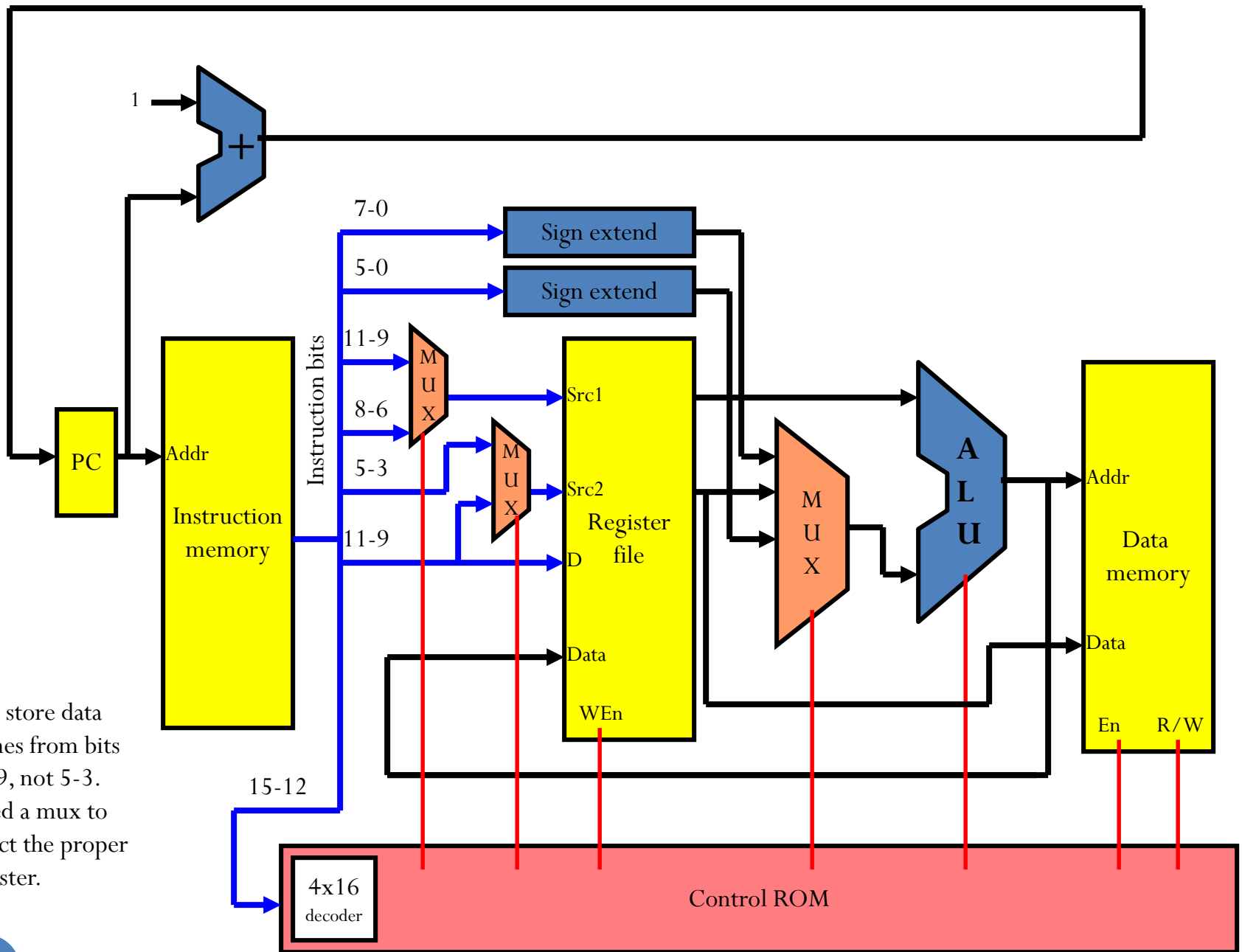

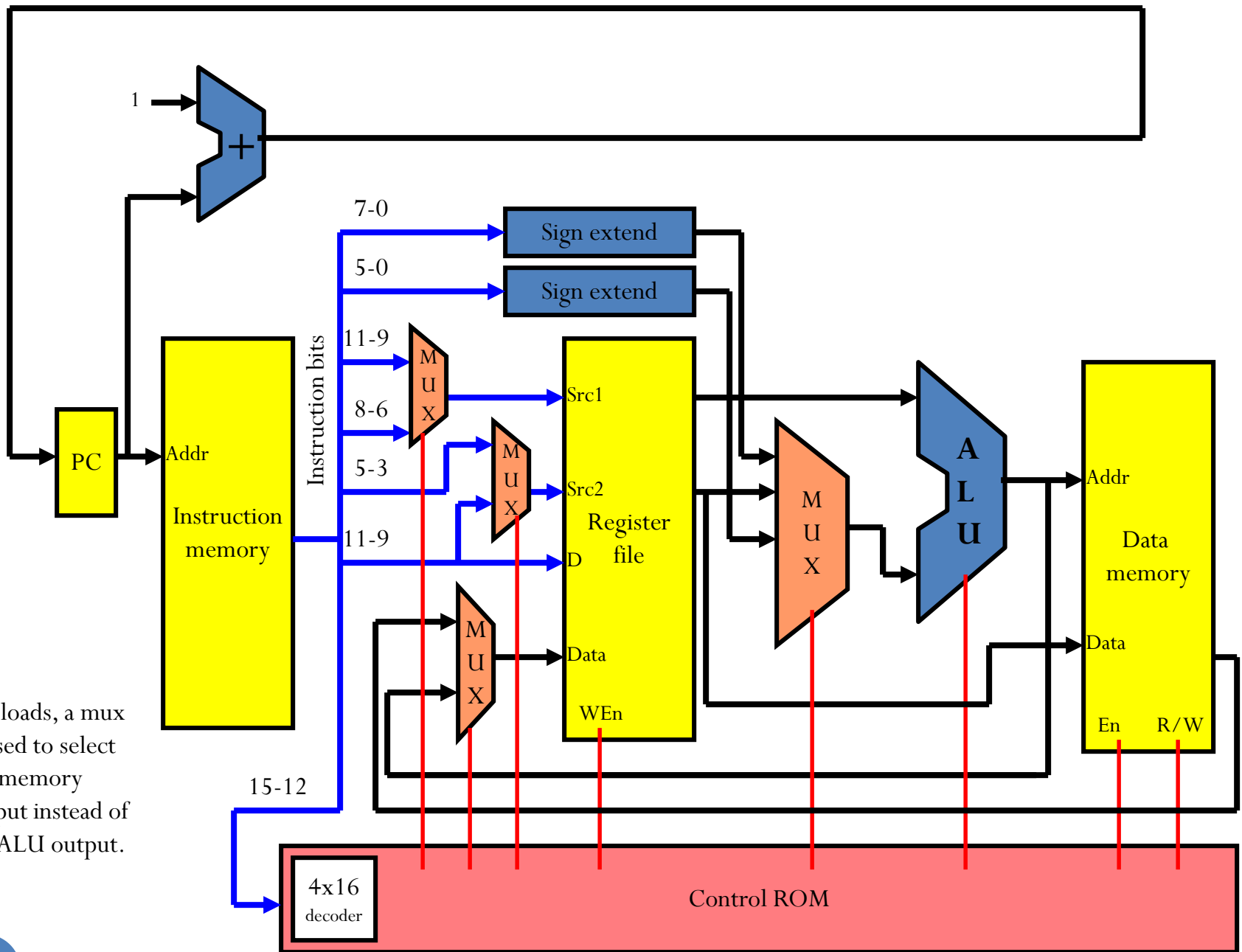The store data comes from bits 11-9, not 5-3. Need a mux to select the proper register.



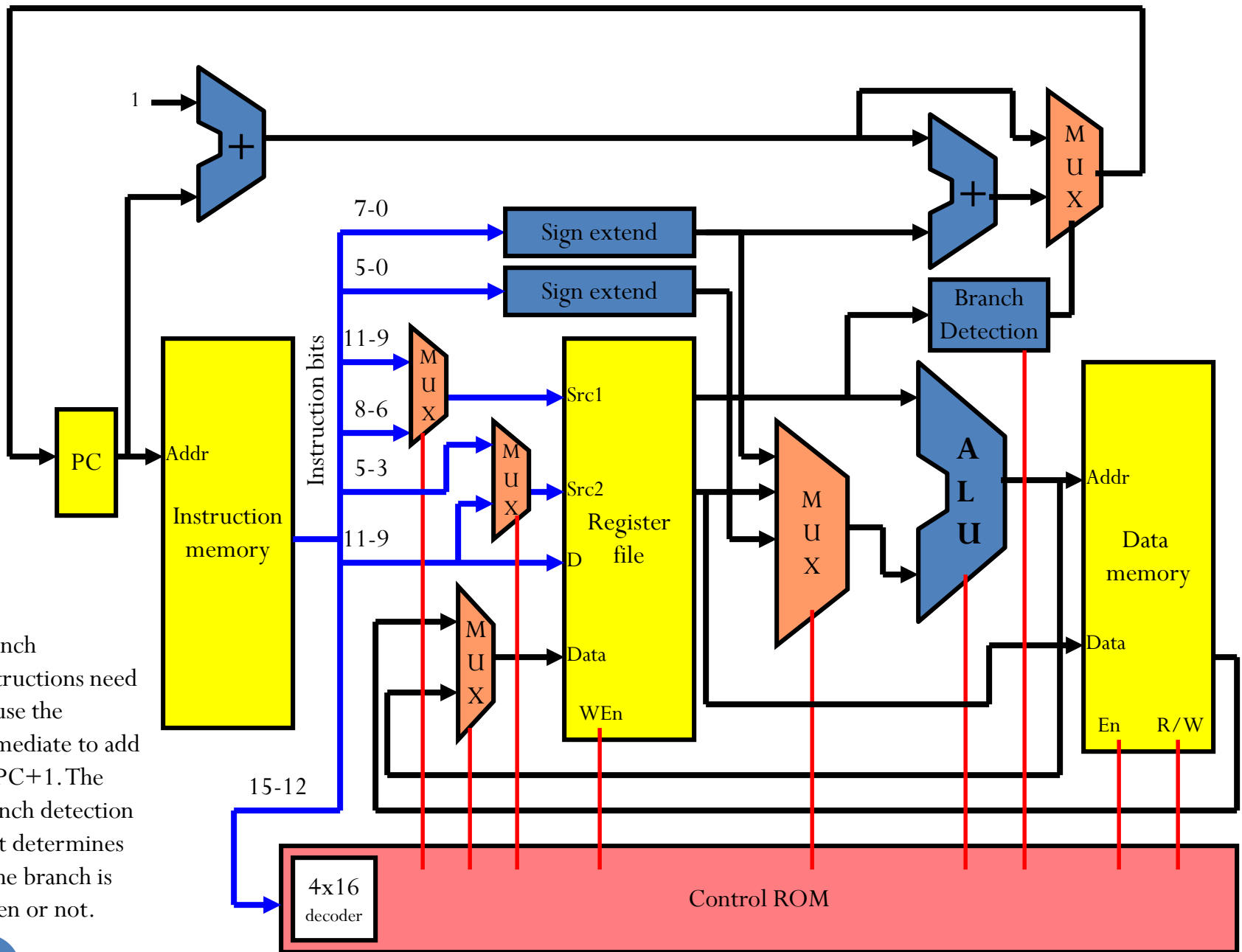For loads, a mux is used to select the memory output instead of the ALU output.




Branch instructions need to use the immediate to add to PC+1. The branch detection unit determines if the branch is taken or not.

Outline

- Introduction to Microarchitecture
- ANNA Datapath
- **ANNA Control**
- Performance
- Pipelining
- Additional Performance Optimizations

Control ROM

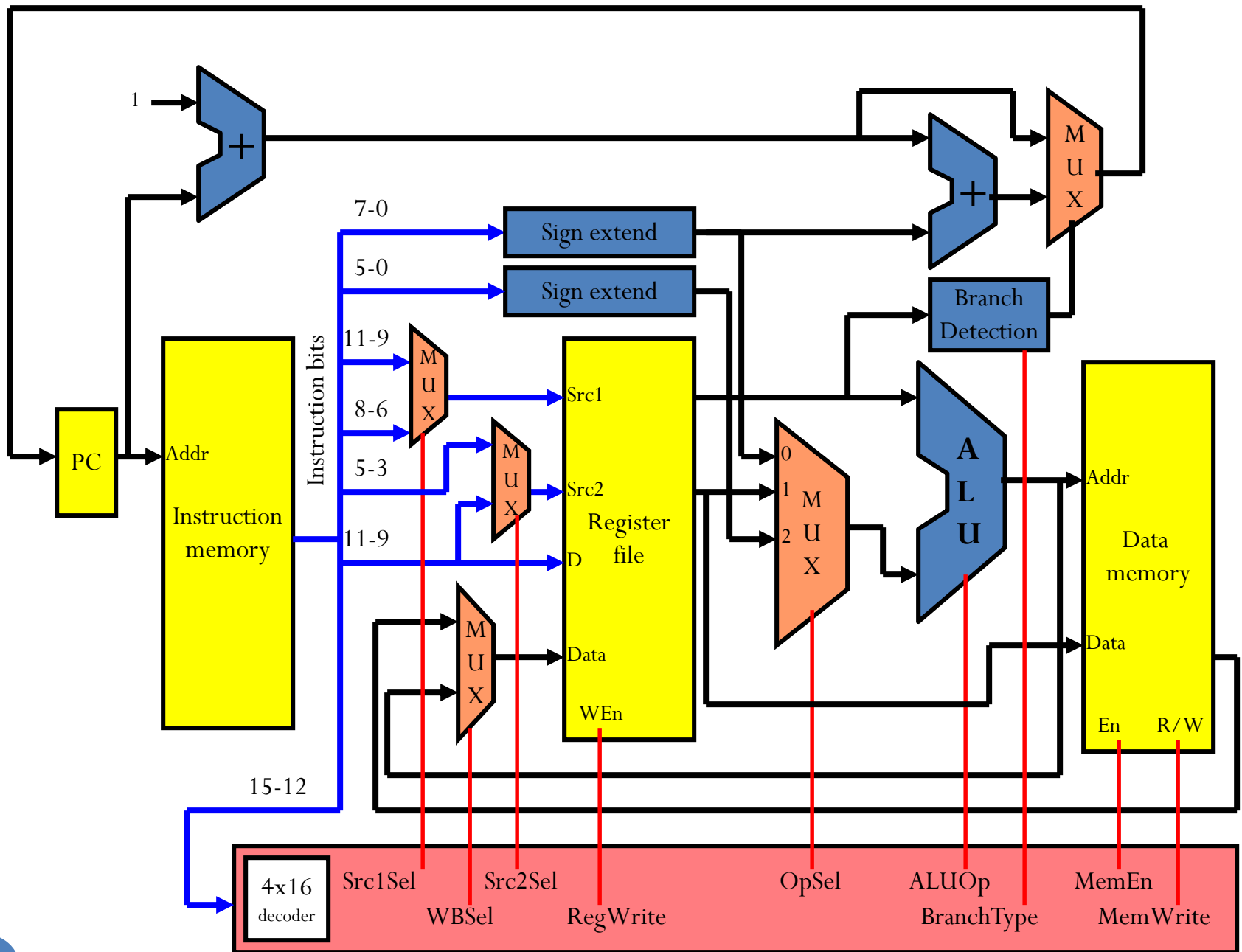- The **control ROM** is a memory that contains an entry for each instruction.
 - Each entry contains the values for the control lines.
- Uses a 4 to 16 decoder to use the opcode to select the proper ROM entry.
- Control lines where the value does not matter are called don't cares (marked with an X).
 - The ROM can use any value.




Control Lines in ANNA

- *Src1Sel*: Selects register to read for src1.
- *Src2Sel*: Selects register to read for src2.
- *WBSel*: Selects where to get data to write back to the register file.
- *RegWrite*: Set if instruction writes to register file.
- *OpSel*: Selects the operand that is used as the second input to the ALU.
- *ALUOp*: Tells the ALU what operation to perform.
- *MemEn*: Set if data memory is enabled.
- *MemWrite*: Set if data memory needs to be written.

Control Lines in ANNA

- For 2 input muxes:
 - 0: top input
 - 1: bottom input
- For the *OpSel* 3 input mux:
 - 0 (00): top input
 - 1 (01): middle input
 - 2 (10): bottom input
 - 3 (11): not used
- *ALUOp*:
 - Arithmetic/logic: three lower opcode bits
 - *addi/lw/sw*: use *add* (000)
- *BranchType*:
 - 00: *bez*
 - 01: *bgz*
 - 11: no branch
- For the enable lines:
 - 0: disabled
 - 1: enabled
- *MemWrite*:
 - 0: read
 - 1: write


Opcode	<i>Src1 Sel</i>	<i>WB Sel</i>	<i>Src2 Sel</i>	<i>Reg Write</i>	<i>OpSel</i>	<i>ALUOp</i>	<i>Branch Type</i>	<i>MemEn</i>	<i>Mem Write</i>
add									
sub									
and									
or									
not									
shf									
addi									
lli									
lui									
lw									
sw									
bez									
bgz									

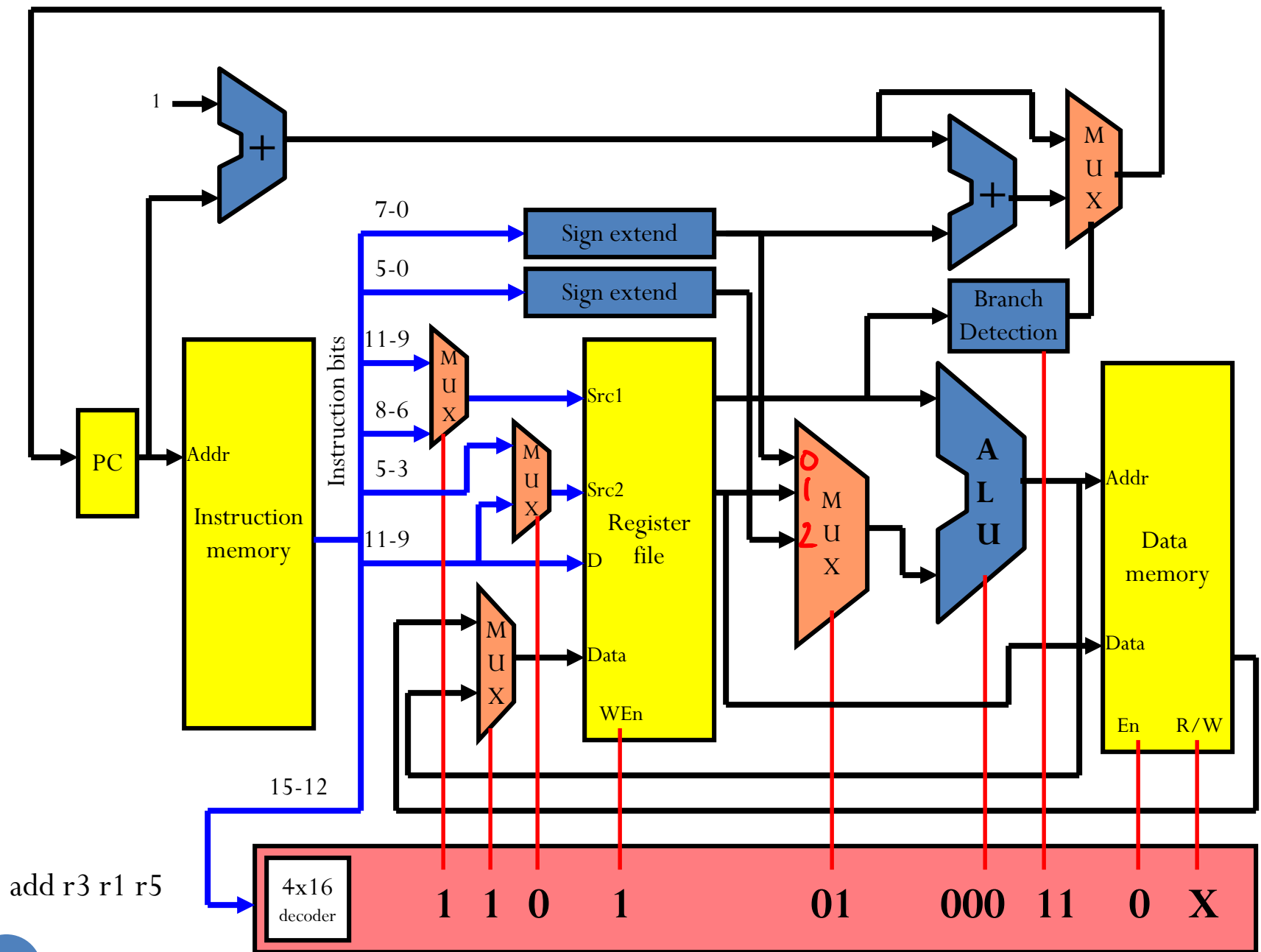

Opcode	<i>Src1 Sel</i>	<i>WB Sel</i>	<i>Src2 Sel</i>	<i>Reg Write</i>	<i>OpSel</i>	<i>ALUOp</i>	<i>Branch Type</i>	<i>MemEn</i>	<i>Mem Write</i>
add	1	1	0	1	01	000	11	0	X
sub									
and									
or									
not									
shf									
addi									
lli									
lui									
lw									
sw									
bez									
bgz									

Opcode	<i>Src1 Sel</i>	<i>WB Sel</i>	<i>Src2 Sel</i>	<i>Reg Write</i>	<i>OpSel</i>	<i>ALUOp</i>	<i>Branch Type</i>	<i>MemEn</i>	<i>Mem Write</i>
add	1	1	0	1	01	000	11	0	X
sub	1	1	0	1	01	001	11	0	X
and	1	1	0	1	01	010	11	0	X
or	1	1	0	1	01	011	11	0	X
not									
shf									
addi									
lli									
lui									
lw									
sw									
bez									
bgz									


[illegible]

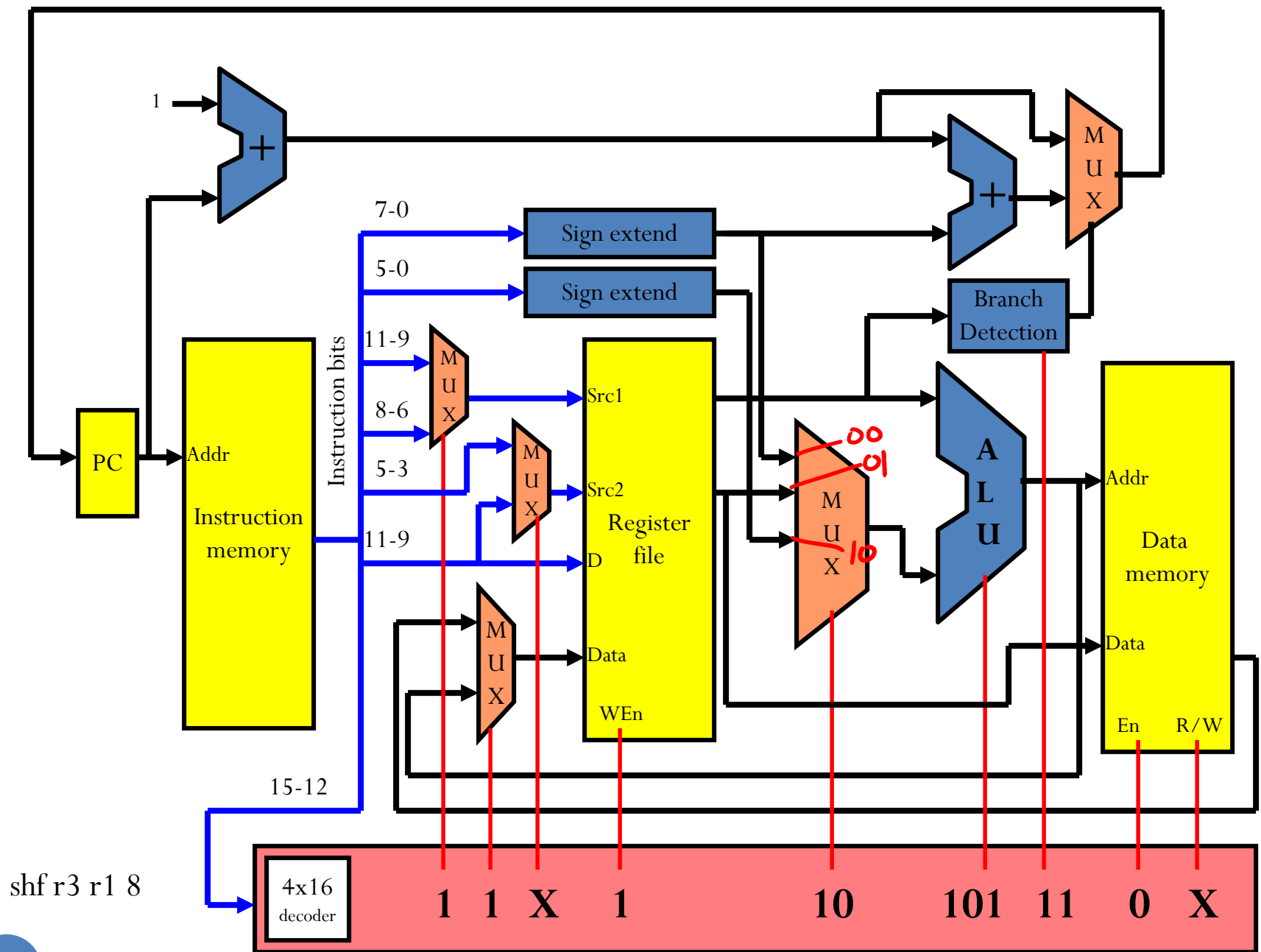


Opcode	Src1 Sel	WB Sel	Src2 Sel	Reg Write	OpSel	ALUOp	Branch Type	MemEn	Mem Write
add	1	1	0	1	01	000	11	0	X
sub	1	1	0	1	01	001	11	0	X
and	1	1	0	1	01	010	11	0	X
or	1	1	0	1	01	011	11	0	X
not	1	1	X	1	X	100	11	0	X
shf	1	1	X	1	10	101	11	0	X
addi									
lli									
lui									
lw									
sw									
bez									
bgz									

Opcode	<i>Src1 Sel</i>	<i>WB Sel</i>	<i>Src2 Sel</i>	<i>Reg Write</i>	<i>OpSel</i>	<i>ALUOp</i>	<i>Branch Type</i>	<i>MemEn</i>	<i>Mem Write</i>
add	1	1	0	1	01	000	11	0	X
sub	1	1	0	1	01	001	11	0	X
and	1	1	0	1	01	010	11	0	X
or	1	1	0	1	01	011	11	0	X
not	1	1	X	1	X	100	11	0	X
shf	1	1	X	1	10	101	11	0	X
addi	1	1	X	1	10	000	11	0	X
lli									
lui									
lw									
sw									
bez									
bgz									


lli r3 0x34

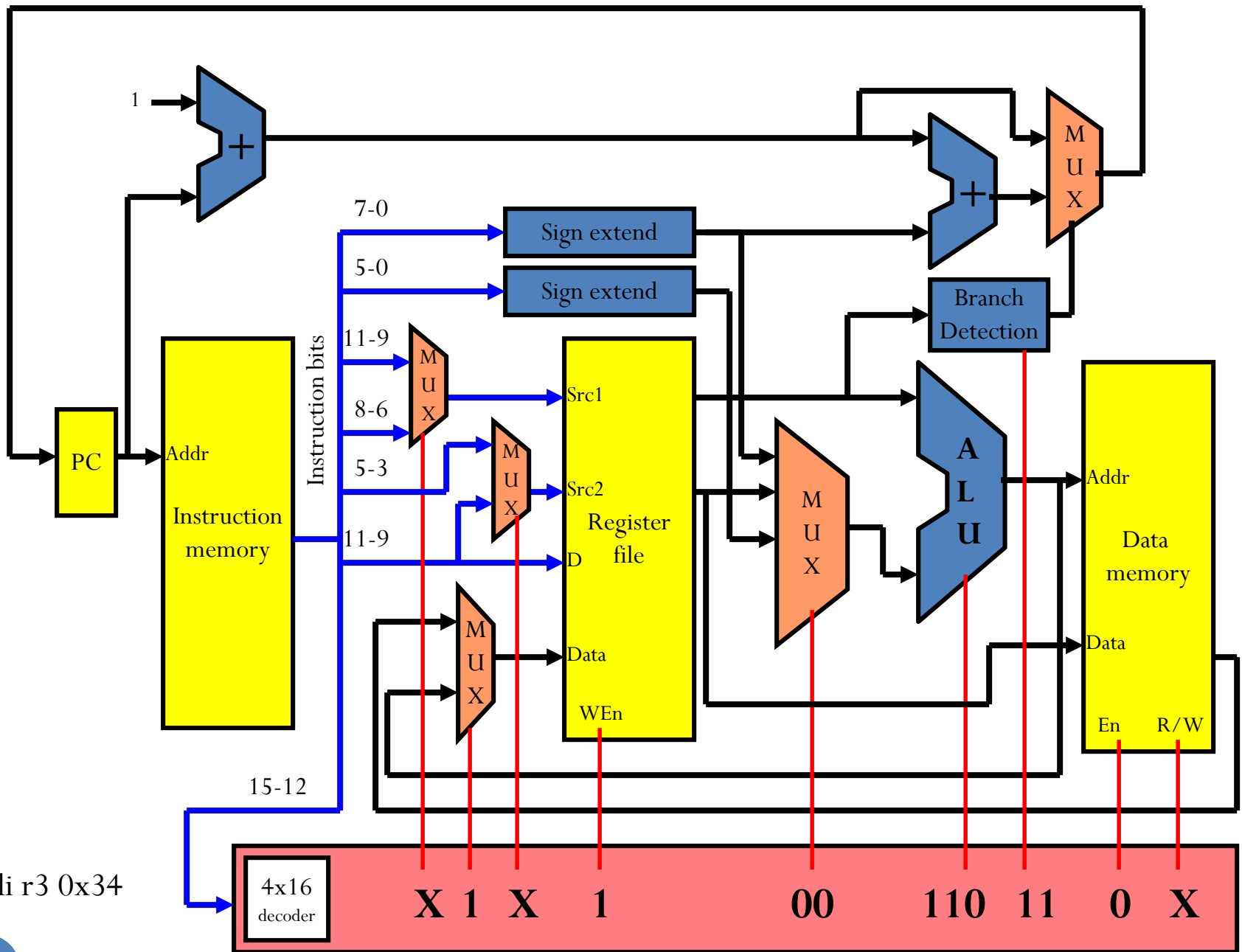


Opcode	Src1 Sel	WB Sel	Src2 Sel	Reg Write	OpSel	ALUOp	Branch Type	MemEn	Mem Write
add	1	1	0	1	01	000	11	0	X
sub	1	1	0	1	01	001	11	0	X
and	1	1	0	1	01	010	11	0	X
or	1	1	0	1	01	011	11	0	X
not	1	1	X	1	X	100	11	0	X
shf	1	1	X	1	10	101	11	0	X
addi	1	1	X	1	10	000	11	0	X
lli	X	1	X	1	00	110	11	0	X
lui									
lw									
sw									
bez									
bgz									

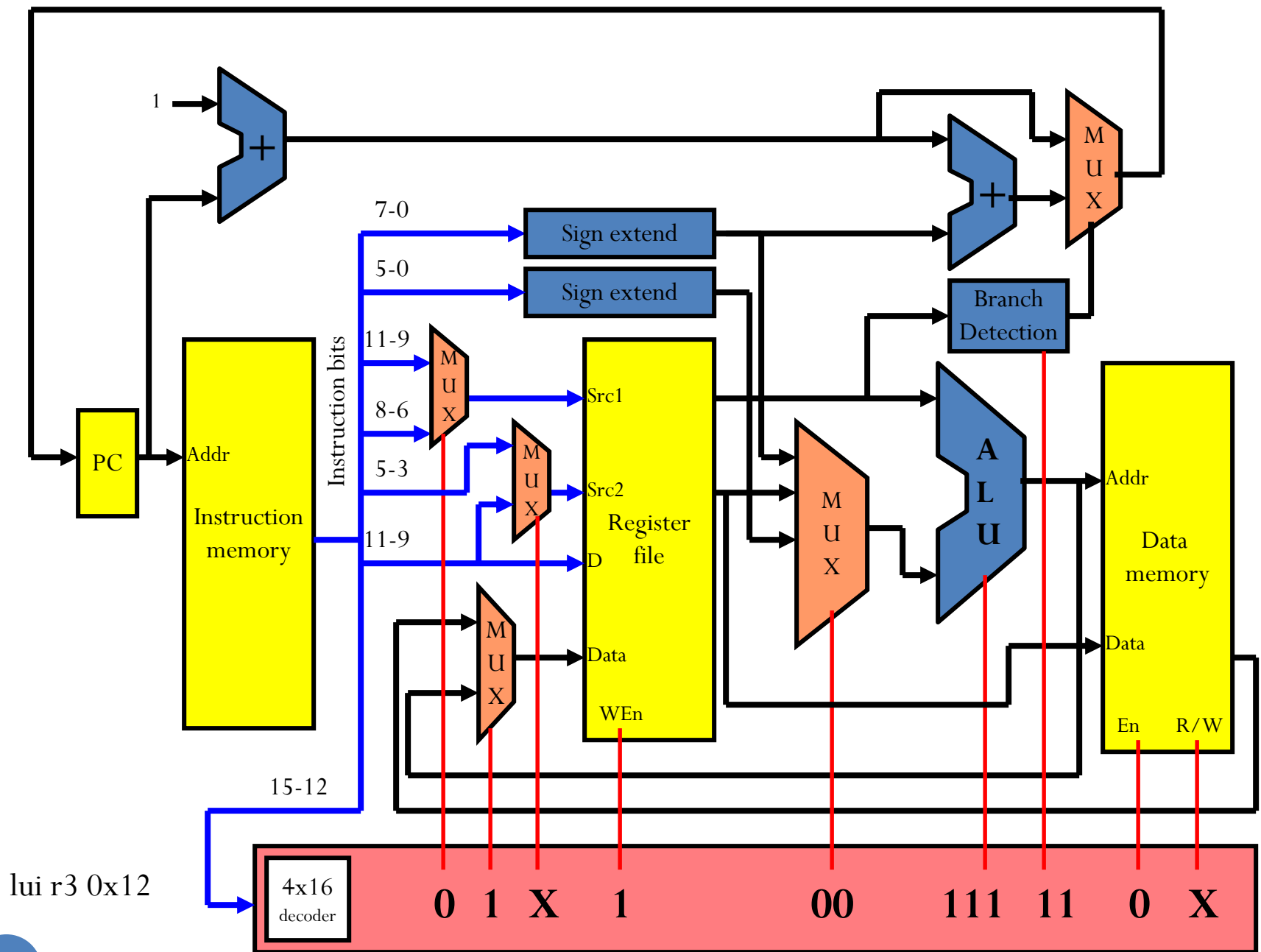


Opcode	Src1 Sel	WB Sel	Src2 Sel	Reg Write	OpSel	ALUOp	Branch Type	MemEn	Mem Write
add	1	1	0	1	01	000	11	0	X
sub	1	1	0	1	01	001	11	0	X
and	1	1	0	1	01	010	11	0	X
or	1	1	0	1	01	011	11	0	X
not	1	1	X	1	X	100	11	0	X
shf	1	1	X	1	10	101	11	0	X
addi	1	1	X	1	10	000	11	0	X
lli	X	1	X	1	00	110	11	0	X
lui	0	1	X	1	00	111	11	0	X
lw									
sw									
bez									
bgz									

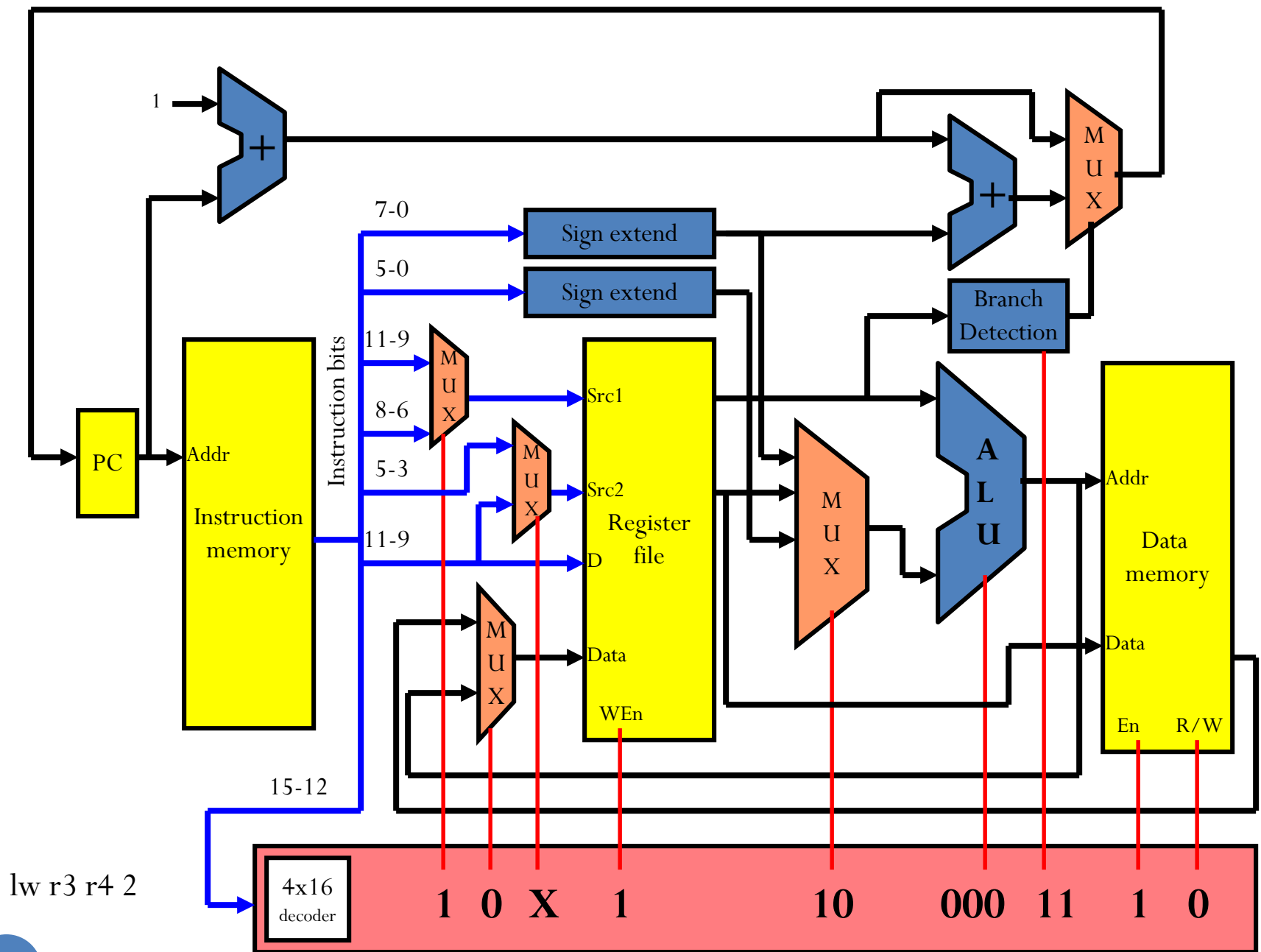

Opcode	Src1 Sel	WB Sel	Src2 Sel	Reg Write	OpSel	ALUOp	Branch Type	MemEn	Mem Write
add	1	1	0	1	01	000	11	0	X
sub	1	1	0	1	01	001	11	0	X
and	1	1	0	1	01	010	11	0	X
or	1	1	0	1	01	011	11	0	X
not	1	1	X	1	X	100	11	0	X
shf	1	1	X	1	10	101	11	0	X
addi	1	1	X	1	10	000	11	0	X
lli	X	1	X	1	00	110	11	0	X
lui	0	1	X	1	00	111	11	0	X
lw	1	0	X	1	10	000	11	1	0
sw									
bez									
bgz									

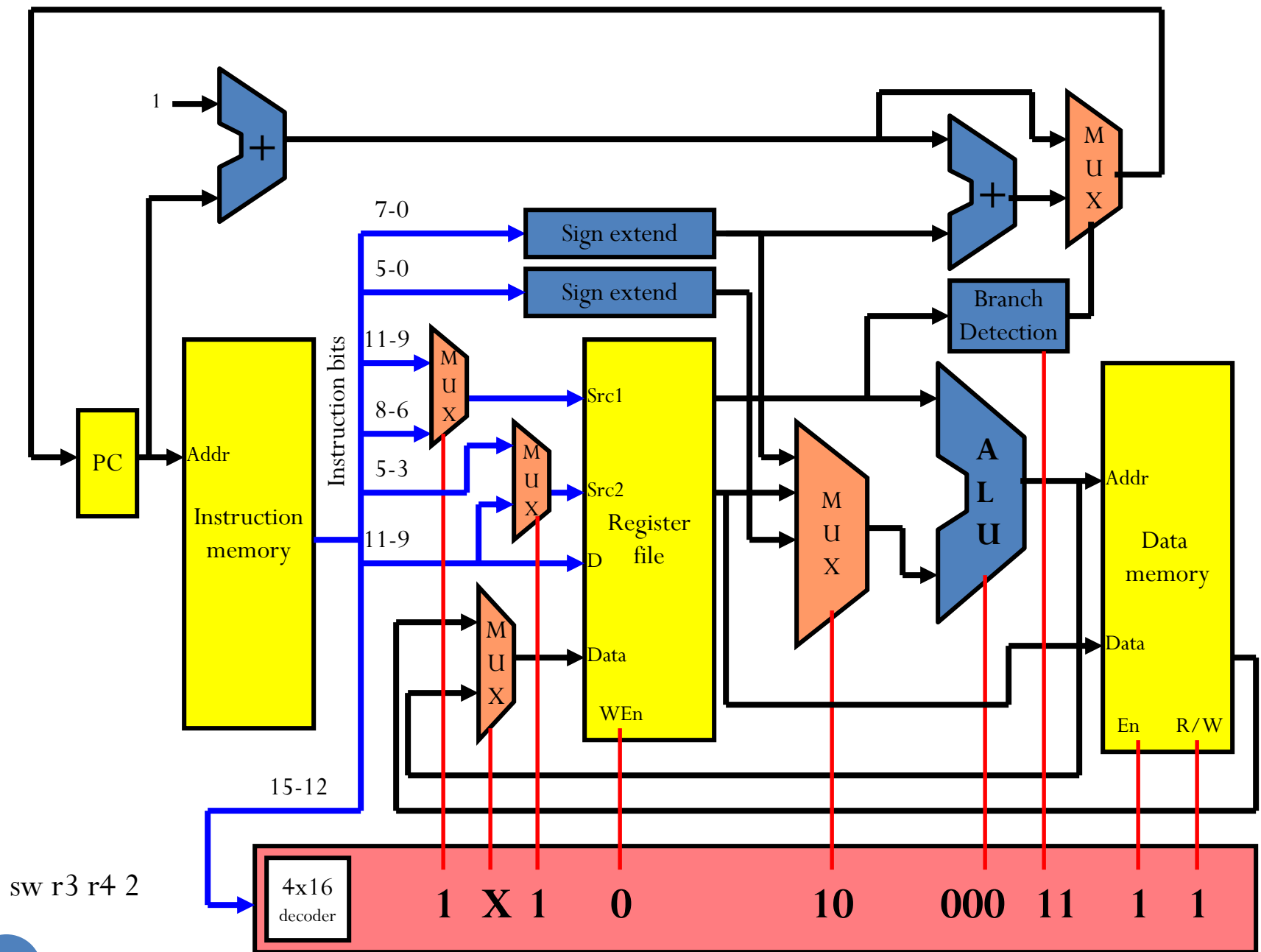

Opcode	Src1 Sel	WB Sel	Src2 Sel	Reg Write	OpSel	ALUOp	Branch Type	MemEn	Mem Write
add	1	1	0	1	01	000	11	0	X
sub	1	1	0	1	01	001	11	0	X
and	1	1	0	1	01	010	11	0	X
or	1	1	0	1	01	011	11	0	X
not	1	1	X	1	X	100	11	0	X
shf	1	1	X	1	10	101	11	0	X
addi	1	1	X	1	10	000	11	0	X
lli	X	1	X	1	00	110	11	0	X
lui	0	1	X	1	00	111	11	0	X
lw	1	0	X	1	10	000	11	1	0
sw	1	X	1	0	10	000	11	1	1
bez									
bgz									

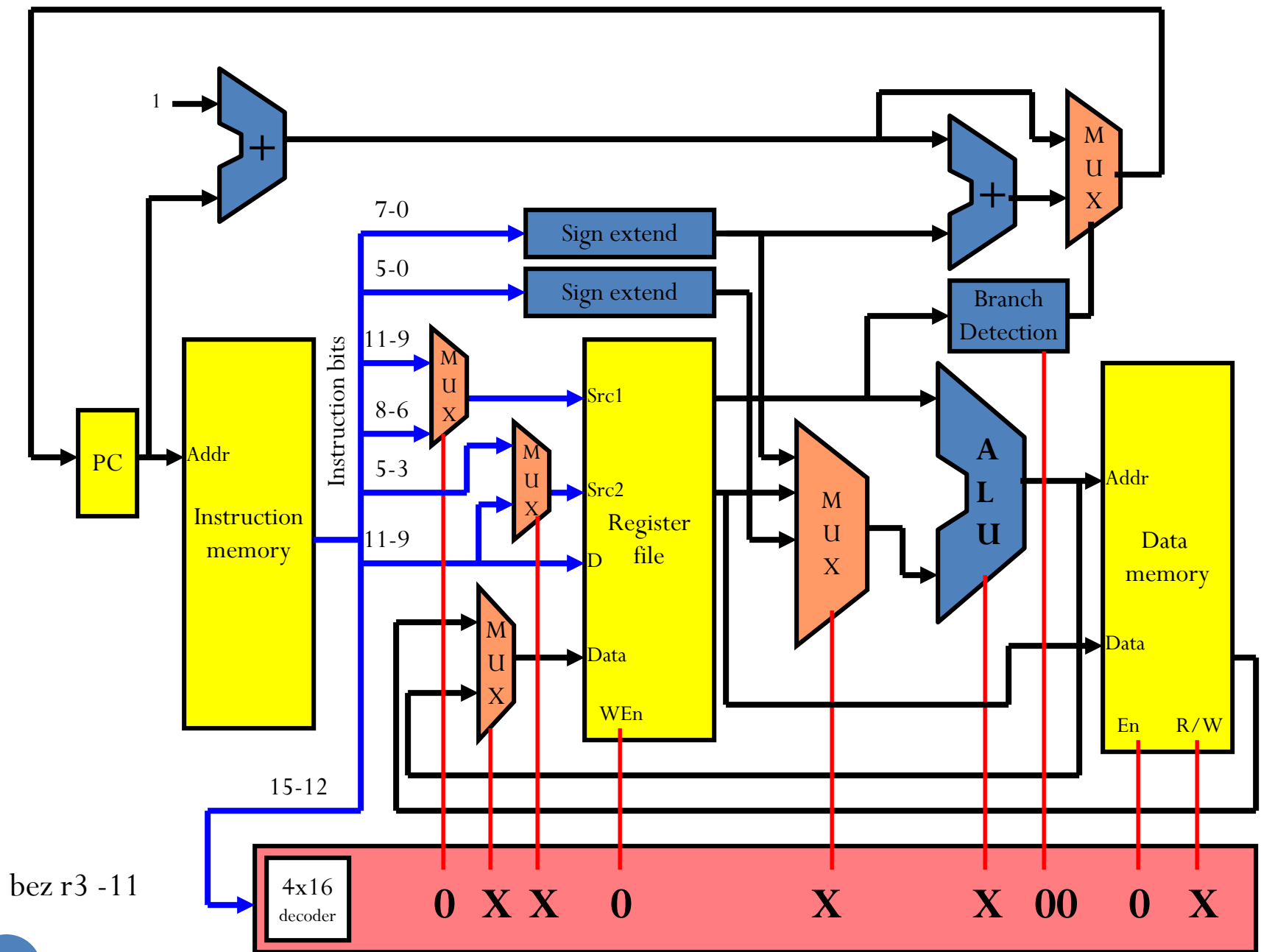

Opcode	Src1 Sel	WB Sel	Src2 Sel	Reg Write	OpSel	ALUOp	Branch Type	MemEn	Mem Write
add	1	1	0	1	01	000	11	0	X
sub	1	1	0	1	01	001	11	0	X
and	1	1	0	1	01	010	11	0	X
or	1	1	0	1	01	011	11	0	X
not	1	1	X	1	X	100	11	0	X
shf	1	1	X	1	10	101	11	0	X
addi	1	1	X	1	10	000	11	0	X
lli	X	1	X	1	00	110	11	0	X
lui	0	1	X	1	00	111	11	0	X
lw	1	0	X	1	10	000	11	1	0
sw	1	X	1	0	10	000	11	1	1
bez	0	X	X	0	X	X	00	0	X
bgz									

Opcode	Src1 Sel	WB Sel	Src2 Sel	Reg Write	OpSel	ALUOp	Branch Type	MemEn	Mem Write
add	1	1	0	1	01	000	11	0	X
sub	1	1	0	1	01	001	11	0	X
and	1	1	0	1	01	010	11	0	X
or	1	1	0	1	01	011	11	0	X
not	1	1	X	1	X	100	11	0	X
shf	1	1	X	1	10	101	11	0	X
addi	1	1	X	1	10	000	11	0	X
lli	X	1	X	1	00	110	11	0	X
lui	0	1	X	1	00	111	11	0	X
lw	1	0	X	1	10	000	11	1	0
sw	1	X	1	0	10	000	11	1	1
bez	0	X	X	0	X	X	00	0	X
bgz	0	X	X	0	X	X	01	0	X

Outline

- Introduction to Microarchitecture
- ANNA Datapath
- ANNA Control
- **Performance**
- Pipelining
- Additional Performance Optimizations

Computer Performance

- What factors are important when considering performance of a computer system?

Average time it takes to process an instruction.

Memory access time

Memory load

Number of instructions

Temperature

Power consumption

Clock speed / frequency

I/O performance

Response time

CPU Time Equation

$$\text{CPU time} = \frac{\text{instructions}}{\text{program}} \times \frac{\text{avg. cycles}}{\text{instruction}} \times \frac{\text{seconds}}{\text{cycle}} = \frac{\text{seconds}}{\text{program}}$$

↑
CPI

Compare systems A + B

$$\frac{\text{time on B}}{\text{time on A}} = n$$

Misleading / Deceptive Statistic Practices

- Only providing clock frequency (often given in GHz).
- Using statistics such as MIPS (Millions of Instructions Per Second) / FLOPS (Floating Point Operations Per Second).
- Selective statistics: Citing only favorable results while omitting others.
- Using biased or irrelevant benchmarks.
- Citing only peak performance numbers while ignoring the average case.
- Vagueness in the use of words like “almost,” “nearly,” “more,” and “less,” in comparing performance data.

Measuring Performance

Measuring performance is hard!

- Hard to come up with a representative and realistic set of benchmarks.
- The compiler and how the program is written factor into the overall time.
- Dependencies on I/O devices, operating systems, libraries, etc.
- Measuring the CPU usage at a fine-grained level can be challenging.
- Different input sizes can drastically change the results.

Single Cycle Datapath

- CPI: 1 (every instruction takes 1 cycle)
- Cycle time (inverse of frequency) is set based on time for longest instruction
- Longest instruction is typically `lw`:
 - Read base address register
 - Compute effective address using ALU
 - Get value from memory
 - Write value from memory to register file
- Problem: All other instructions waste time.

Multiple Cycle Datapath

- Instructions can take multiple cycles to execute.
- Longer instructions take more cycles; shorter instructions take fewer cycles.
- Cycle time is shorter → less work per cycle
- Is it faster than single cycle?

Lower cycle time → decrease time

Higher CPI → increases time

Multiple Cycle vs. Single Cycle

- Loads and stores take longer than other instructions because of the additional memory access for data.
 - Single cycle: cycle time based on load instruction execution time.
 - Multiple cycle: may take longer than single cycle because the division into cycles may not be clean.
- Instructions with only register operands will typically be faster in a multiple cycle implementation.
 - Single cycle: will sit idle for some portion of the cycle
 - Multiple cycle: will take fewer cycles than load and store
- Is multiple cycle faster than single cycle?
 - depends on number of loads and stores

Most Frequently Executed Instructions (SPECInt Benchmarks)

- | | | |
|----|--------------------|-----|
| 1. | load | 22% |
| 2. | sub / compare | 21% |
| 3. | conditional branch | 20% |
| 4. | store | 12% |
| 5. | add / move | 12% |
| 6. | and | 6% |

Strikes: **X** **X** **X**

All other instruction types 1% or less per type

Class Problem

- Single cycle time: 45 ns
- Multiple cycle time: 10 ns
- Multiple cycle implementation:

- lw:

5 cycles

- sw:

4 cycles

- all other instructions: 3 cycles

- Determine how long it would take to run the same 100 instruction program on each implementation.
 - Use the instruction frequencies from the previous slide.

Single cycle: $100 \text{ inst} \left(\frac{1 \text{ cycle}}{\text{inst}} \right) \left(\frac{45 \text{ ns}}{1 \text{ cycle}} \right) = 4500 \text{ ns}$


Multiple cycle: $100 \text{ inst} \left(\frac{3.56 \text{ cycles}}{\text{inst}} \right) \left(\frac{10 \text{ ns}}{1 \text{ cycle}} \right) = 3560 \text{ ns}$

Multiple cycle CPI: $(0.22 \times 5) + (0.12 \times 4) + (0.66 \times 3) = 3.56$


Outline

- Introduction to Microarchitecture
- ANNA Datapath
- ANNA Control
- Performance
- **Pipelining**
- Additional Performance Optimizations


Pipelining

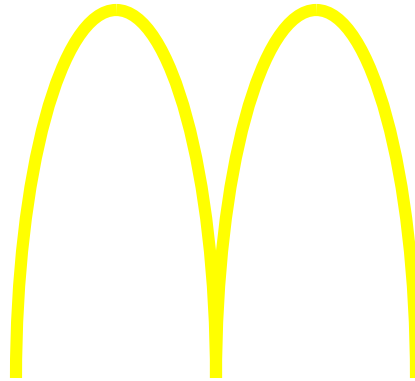


order

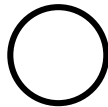

pay

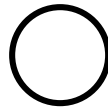

pickup

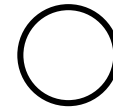


Pipelining



add






and

lw

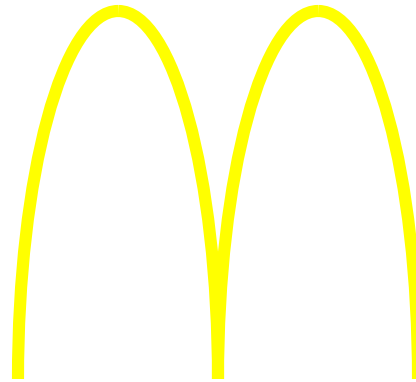

icroprocessor

fetch decode ALU mem writeback

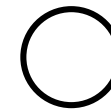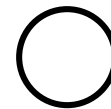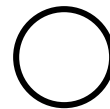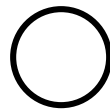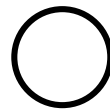

lw

sub

add


sw

lui

add


Pipelined Implementation of ANNA

- Break the execution of the instructions into cycles.
 - Similar to multiple cycle datapath.
- Design a separate datapath stage for the execution performed during each cycle.
- Instructions can overlap execution.
 - Different instructions can be in different cycles.
- Build pipeline registers to communicate between different stages.

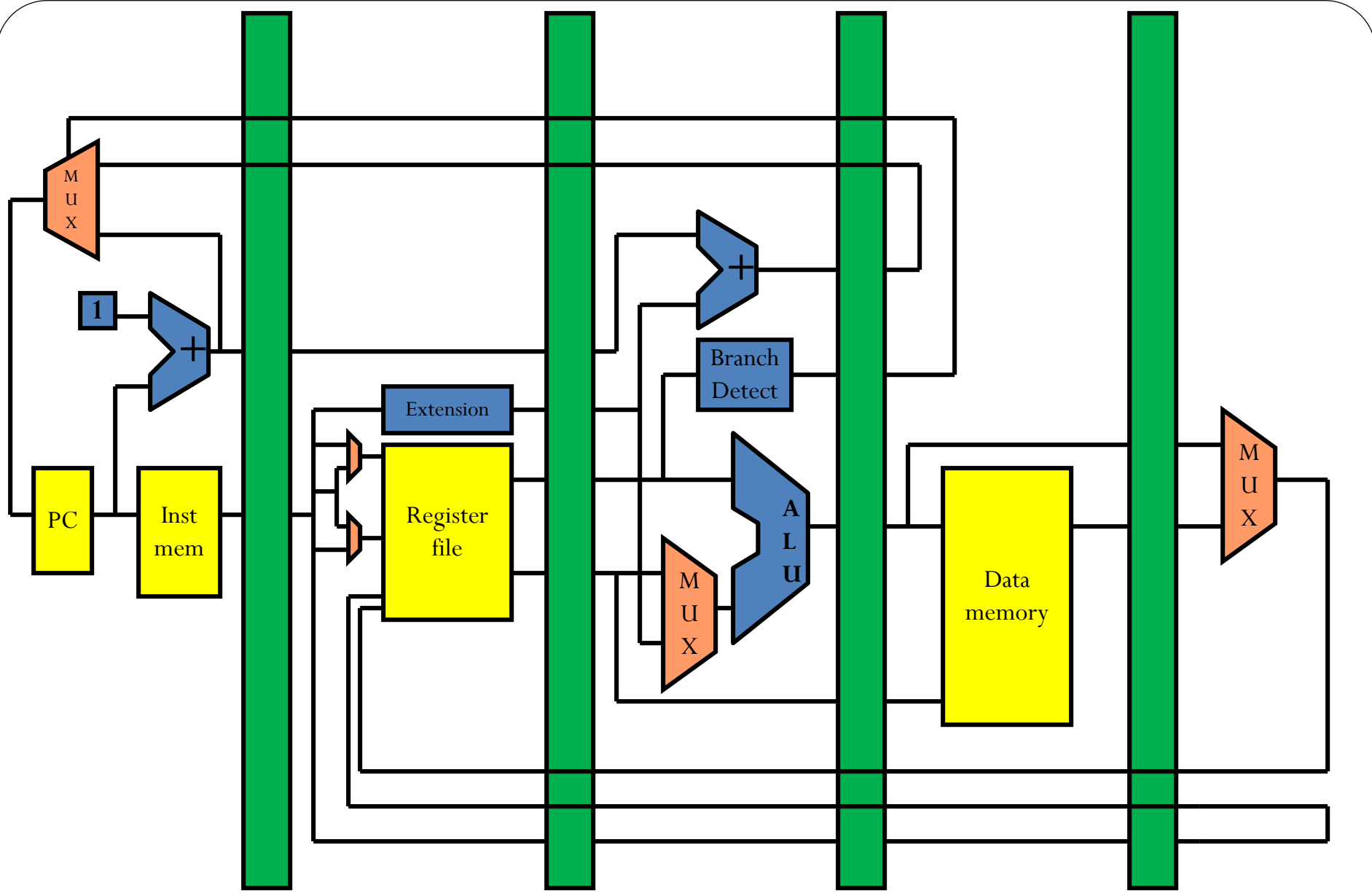

Stage 1: Fetch (IF)

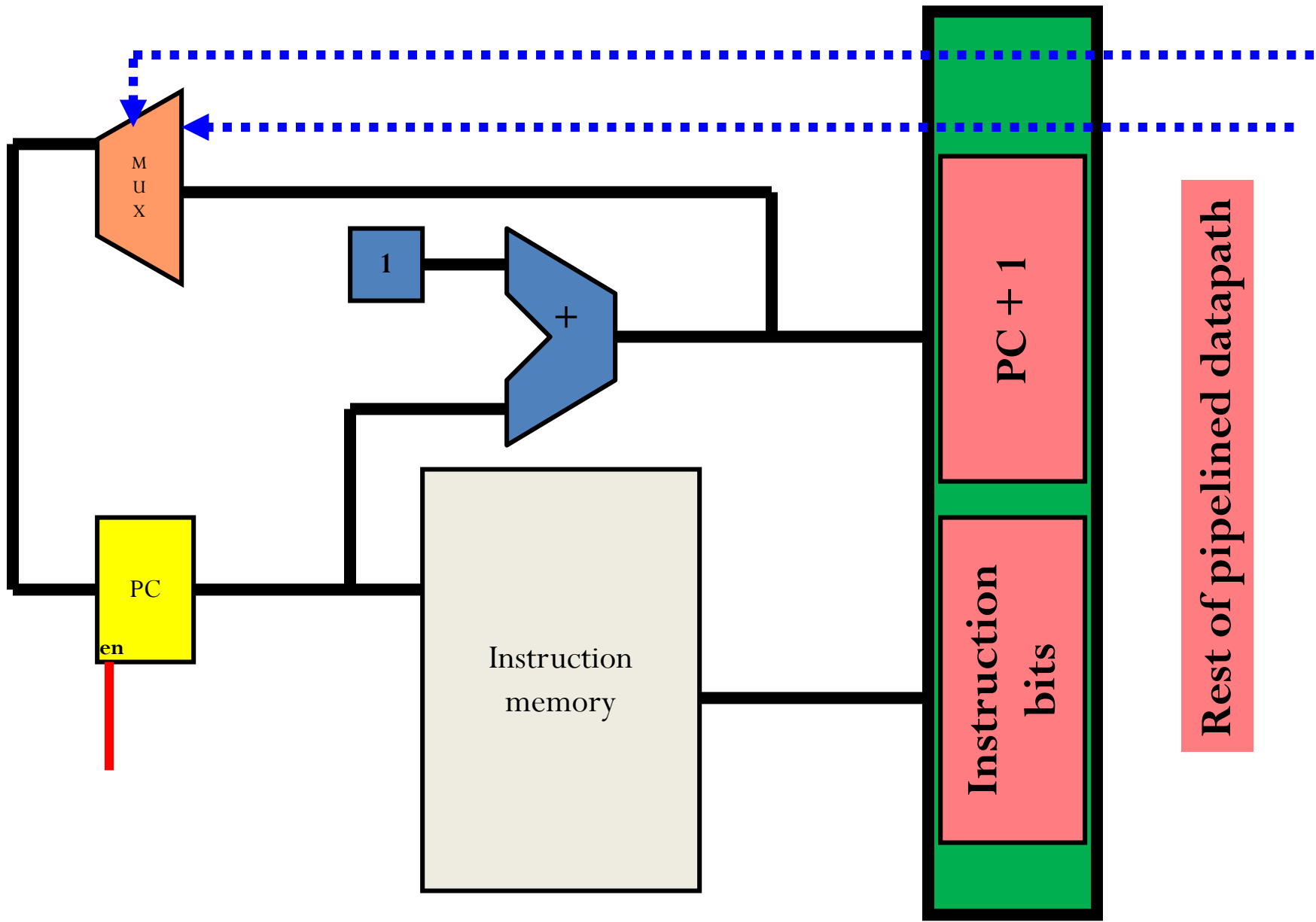- Design a datapath that can fetch an instruction from memory every cycle.
 - Use PC to index instruction memory.
 - Increment the PC (assume no branches for now).
- Write everything needed to complete execution to the pipeline register (IF/ID).
 - The next stage will read this pipeline register.
 - Note that pipeline register must be edge triggered.




IF / ID

Pipeline register

Stage 2: Decode (ID)

- Reads the IF/ID pipeline register and decodes instruction.
 - Decode is easy: pass opcode to later stages and let them figure out what to do.
- Reads register file.
- Determine immediate (based on instruction).
- Write everything needed to complete execution to the pipeline register (**ID/EX**):
 - register values
 - immediate
 - opcode and destination register number (could pass entire instruction)
 - PC+1 (even though decode doesn't use it)


Stage 1: Fetch datapath

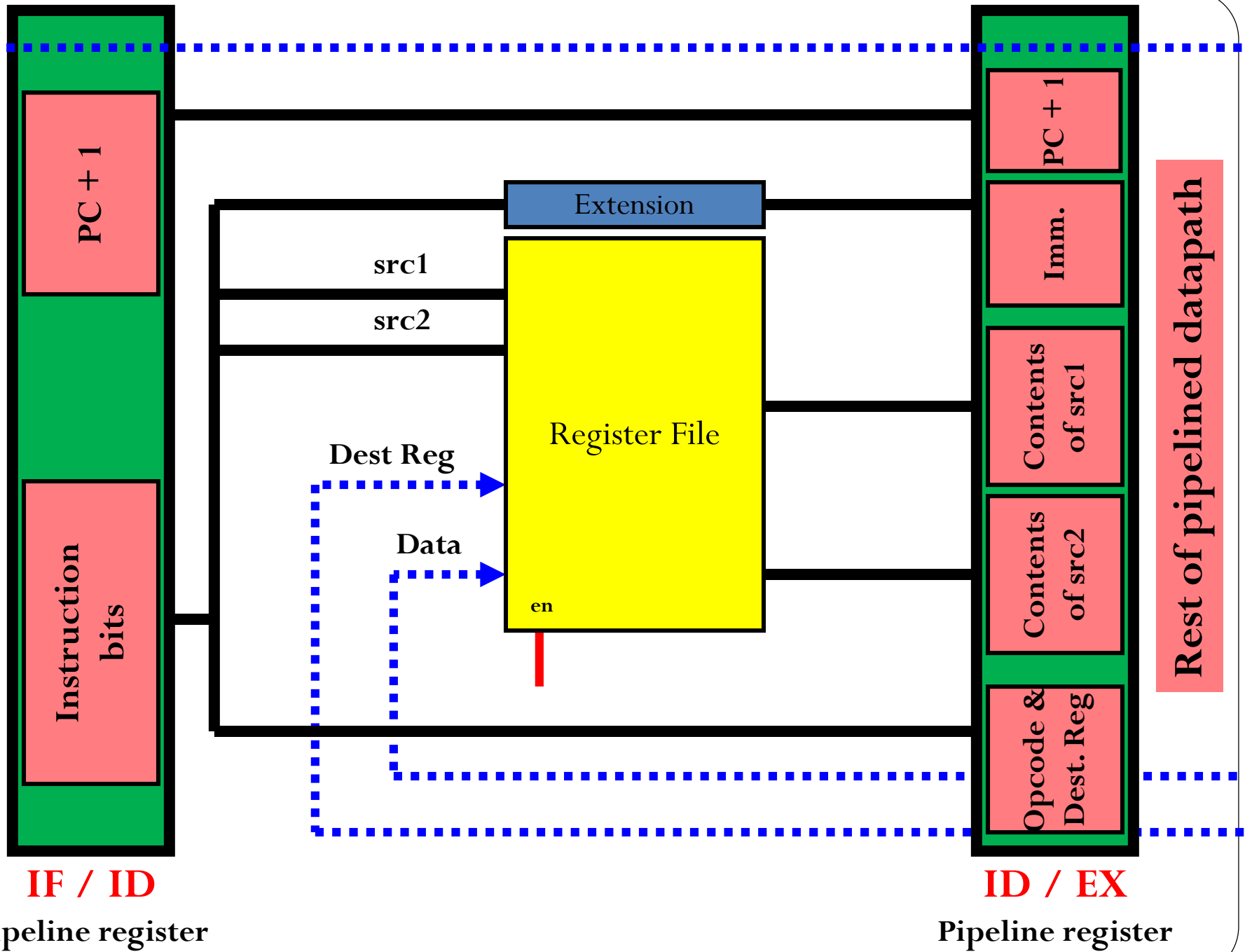

Stage 3: Execute (EX)

- Performs the proper ALU operation for the instruction specified and the values present in the ID/EX pipeline register.
- Calculates target address in case this is a branch.
 - Also determines if branch is taken or not.
- Write everything needed to complete execution to the pipeline register (**EX/MEM**):
 - ALU result
 - contents of register src2 (store data)
 - target address
 - result from branch detection unit
 - instruction bits for opcode and destination register


Stage 2: Decode datapath

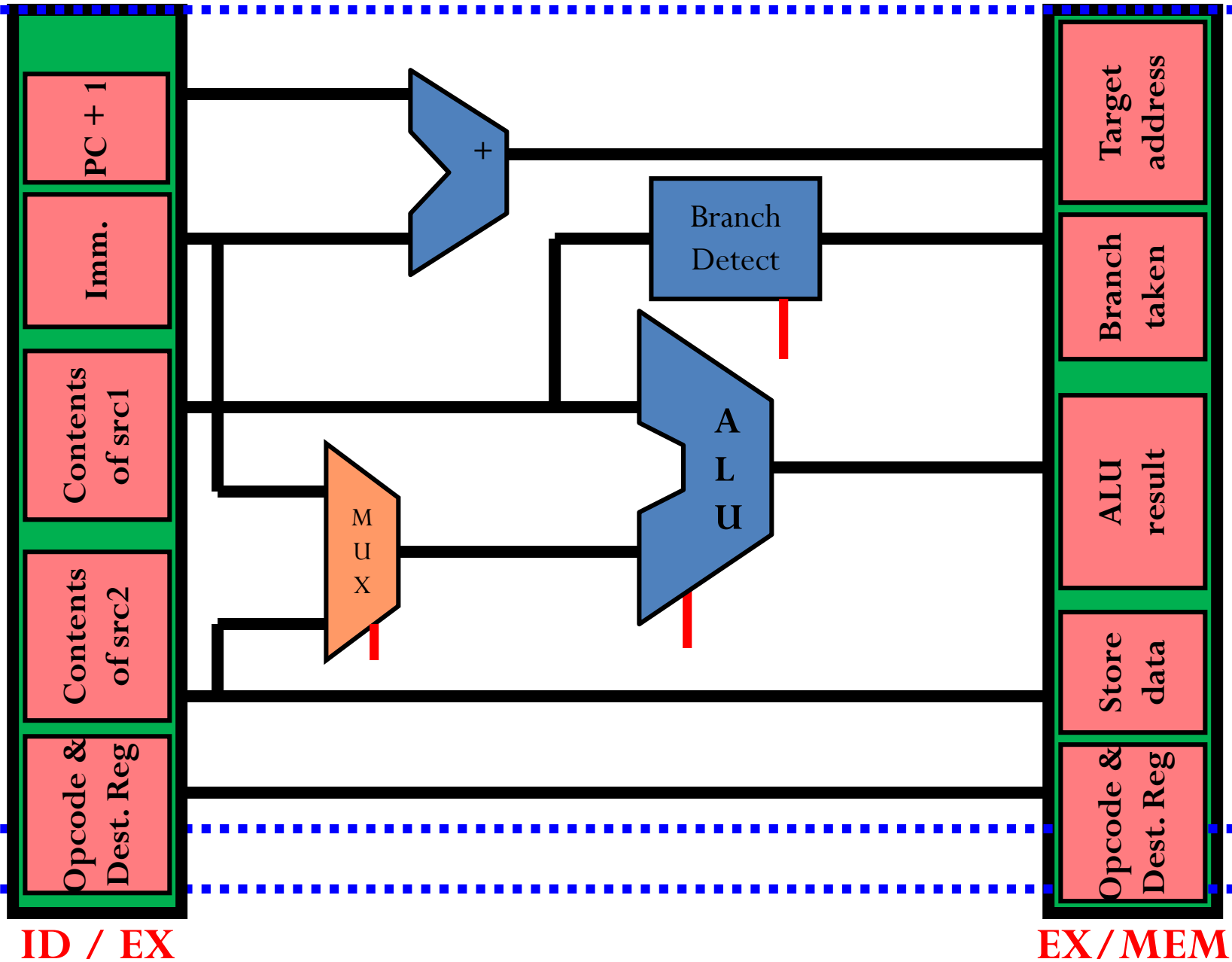

Rest of pipelined datapath

Stage 4: Memory Operation (MEM)


- Performs the proper memory operation based on the instruction in EX/MEM pipeline register.
- Also resolves taken branches (more later).
- Nothing is done for ALU operations.
- Write everything needed to complete execution to the pipeline register (**MEM/WB**)
 - ALU result
 - data from memory (result of load)
 - instruction bits for opcode and destination register

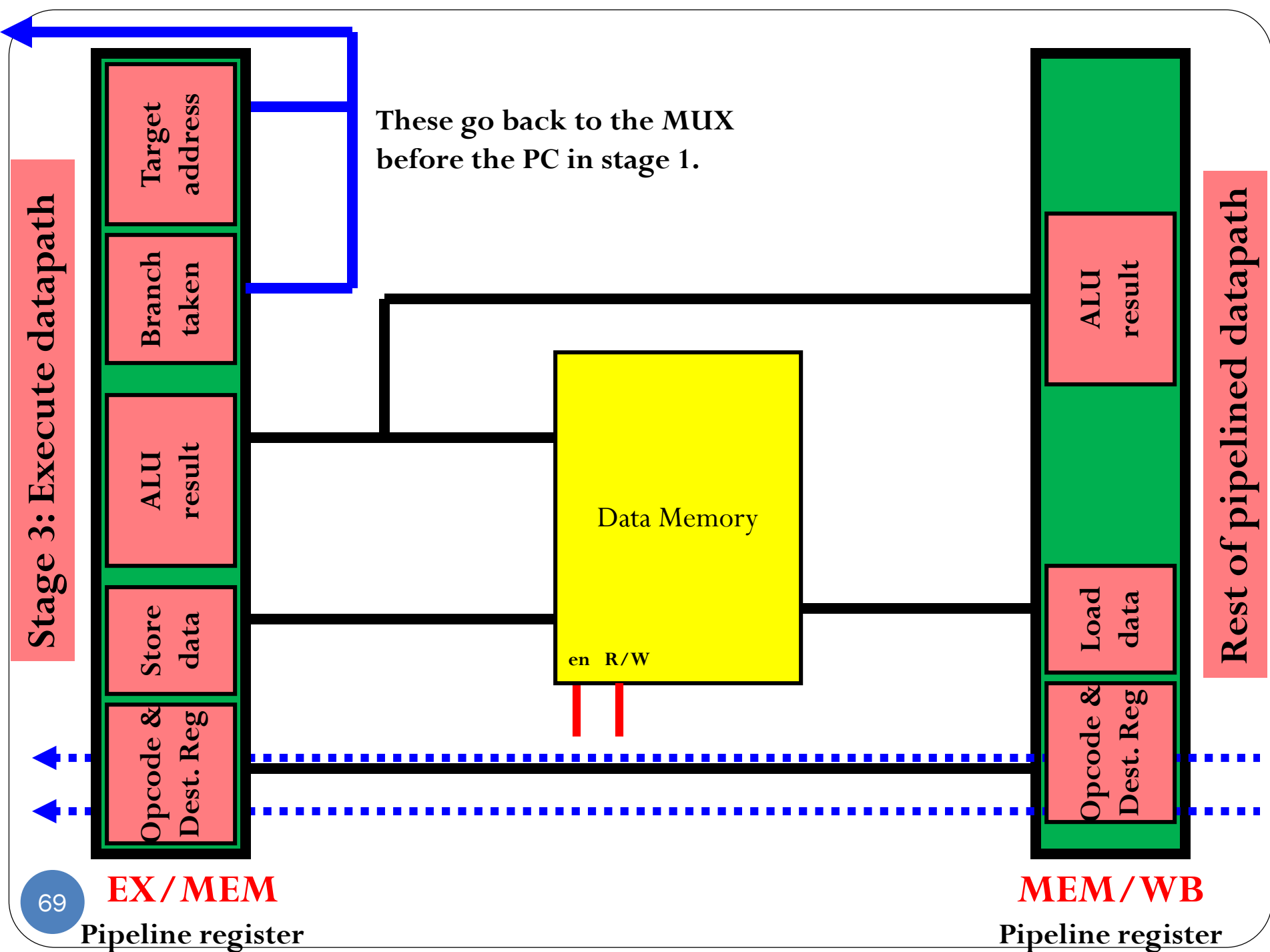

Stage 5: Write back (WB)

- Completes execution of instruction by writing a value back to the register file.
- Instructions that do not write back to the register file do not do anything.

Stage 4: Memory datapath

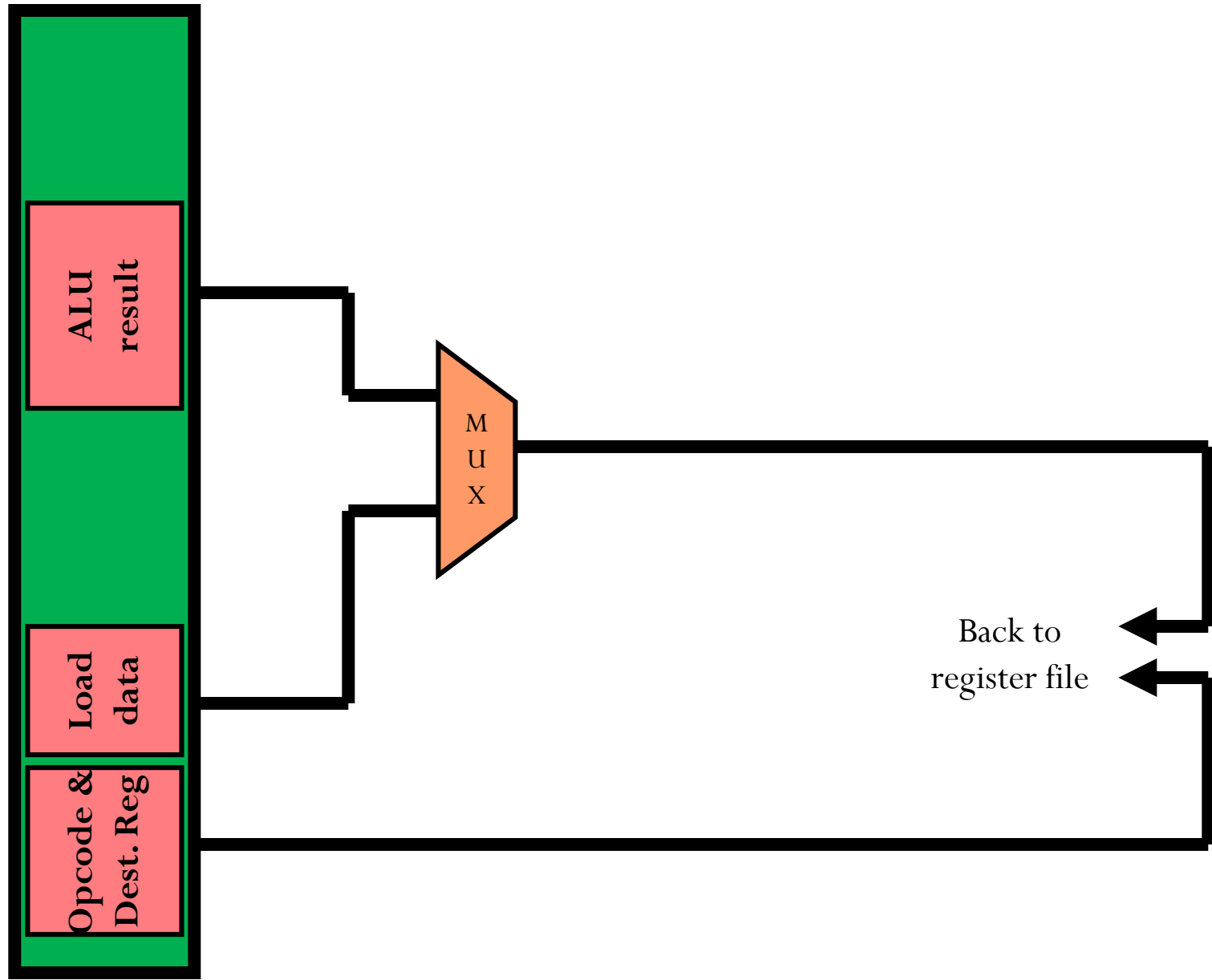

MEM/WB

Pipeline register

Example: Sample program

Run the following program on pipeline ANNA processor:


```
add r1 r2 r3          // PC = 20
```

```
lw r4 r5 1
```

```
and r6 r2 r3
```

```
sw r7 r5 9
```

```
or r4 r3 r7
```

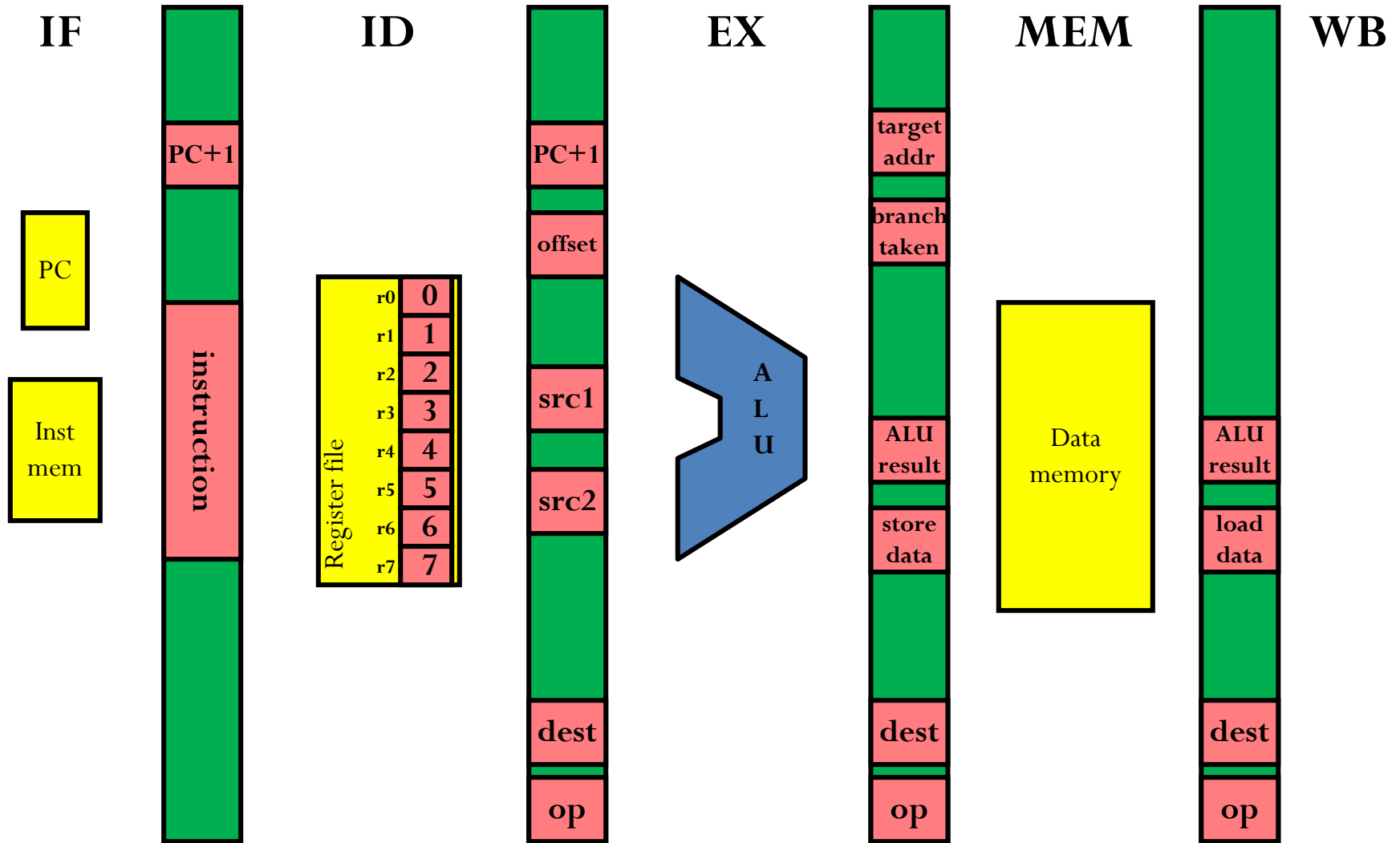
IF

ID



EX

MEM

WB

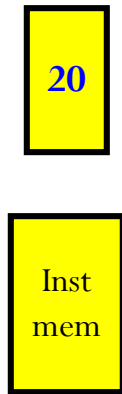

Register file	r0	0
	r1	1
	r2	2
	r3	3
	r4	4
	r5	5
	r6	6
	r7	7

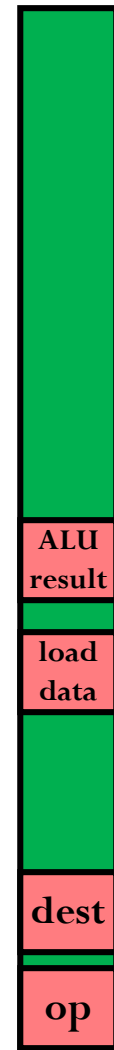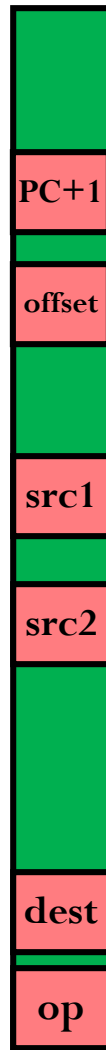

add r1 r2 r3


IF

ID




EX

MEM

WB

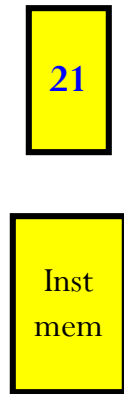

Register file	r0	0
	r1	1
	r2	2
	r3	3
	r4	4
	r5	5
	r6	6
	r7	7

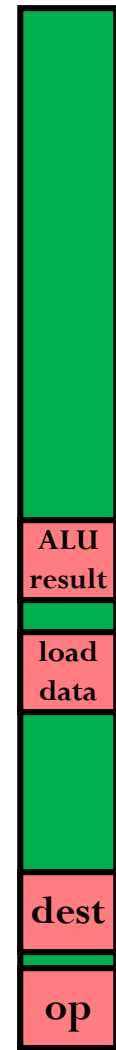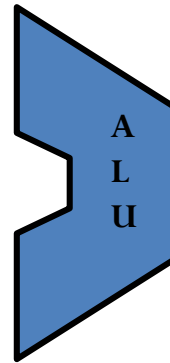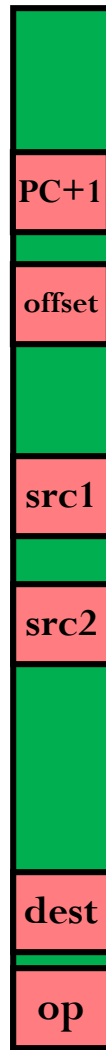

lw r4 r5 1

add r1 r2 r3


IF

ID



EX

MEM

WB

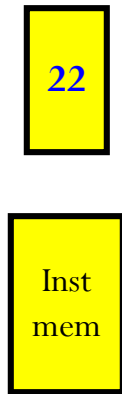

Register file	r0	0
	r1	1
	r2	2
	r3	3
	r4	4
	r5	5
	r6	6
	r7	7

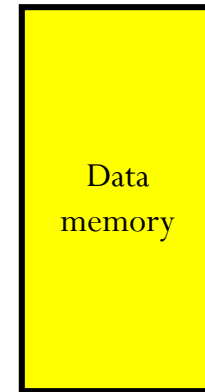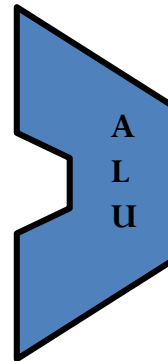

and r6 r2 r3

lw r4 r5 1

add r1 r2 r3


IF

ID






EX

MEM

WB

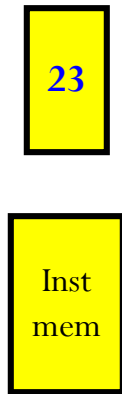

Register file	r0	0
	r1	1
	r2	2
	r3	3
	r4	4
	r5	5
	r6	6
	r7	7

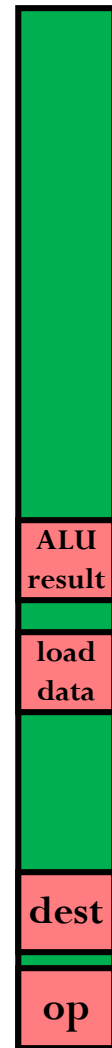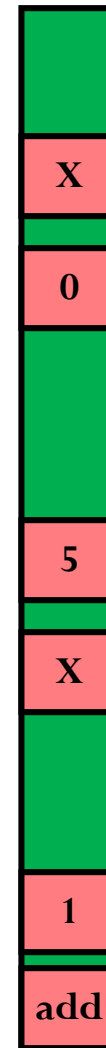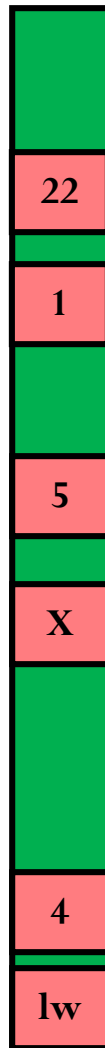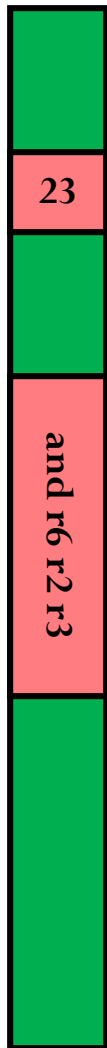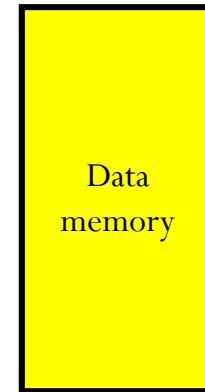

sw r7 r5 9

and r6 r2 r3

lw r4 r5 1

add r1 r2 r3


IF

ID

EX

MEM

WB

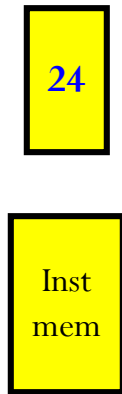

Register file	r0	0
	r1	5
	r2	2
	r3	3
	r4	4
	r5	5
	r6	6
	r7	7



or r4 r3 r7

sw r7 r5 9

and r6 r2 r3

lw r4 r5 1

add r1 r2 r3

IF

ID

EX

MEM


WB

PC



Inst
mem

Register file	r0	0
	r1	5
	r2	2
	r3	3
	r4	88
	r5	5
	r6	6
	r7	7


or r4 r3 r7

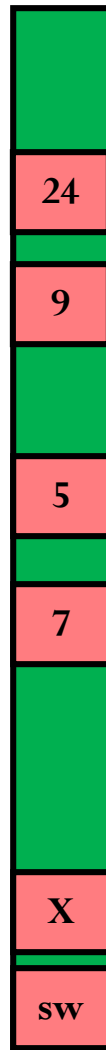

sw r7 r5 9

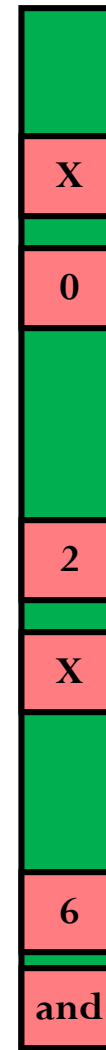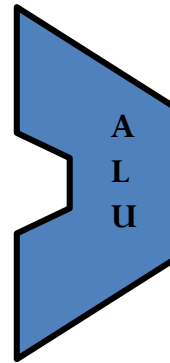

and r6 r2 r3

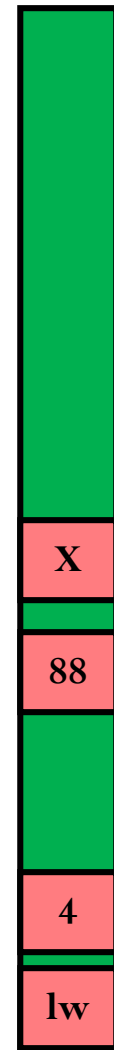

lw r4 r5 1

IF

ID

EX

MEM

WB

PC

Inst
mem

Register file	r0	0
	r1	5
	r2	2
	r3	3
	r4	88
	r5	5
	r6	2
	r7	7

A
L
U

Data
memory

or r4 r3 r7

sw r7 r5 9

and r6 r2 r3

IF

ID

EX

MEM

WB

PC

Inst
mem

Register file	r0	0
	r1	5
	r2	2
	r3	3
	r4	88
	r5	5
	r6	2
	r7	7

A
L
U

Data
memory

or r4 r3 r7

sw r7 r5 9

IF

ID





EX

MEM

WB



Register file	r0	0
	r1	5
	r2	2
	r3	3
	r4	7
	r5	5
	r6	2
	r7	7

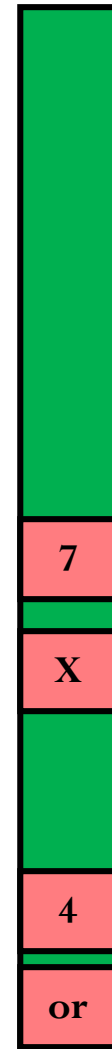  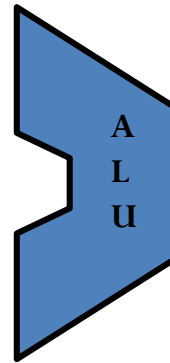

or r4 r3 r7

Time Graph

cycles

Time:	1	2	3	4	5	6	7	8	9	10	11	12	13
add r1 r2 r3	IF	ID	EX	ME	WB								
lw r4 r5 1		IF	ID	EX	ME	WB							
and r6 r2 r3			IF	ID	EX	ME	WB						
sw r7 r5 9				IF	ID	EX	ME	WB					
or r4 r3 r7					IF	ID	EX	ME	WB				


$$CPI = \frac{9 \text{ cycles}}{5 \text{ instructions}} = 1.8$$


Ignoring startup, CPI ≈ 1 .


Problem: Dependent Instructions

What about this sequence of instructions?

```
add r1 r2 r3  
sub r4 r5 r1
```

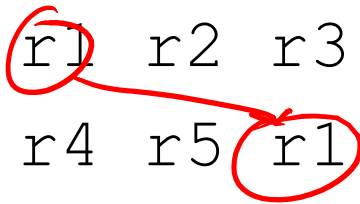

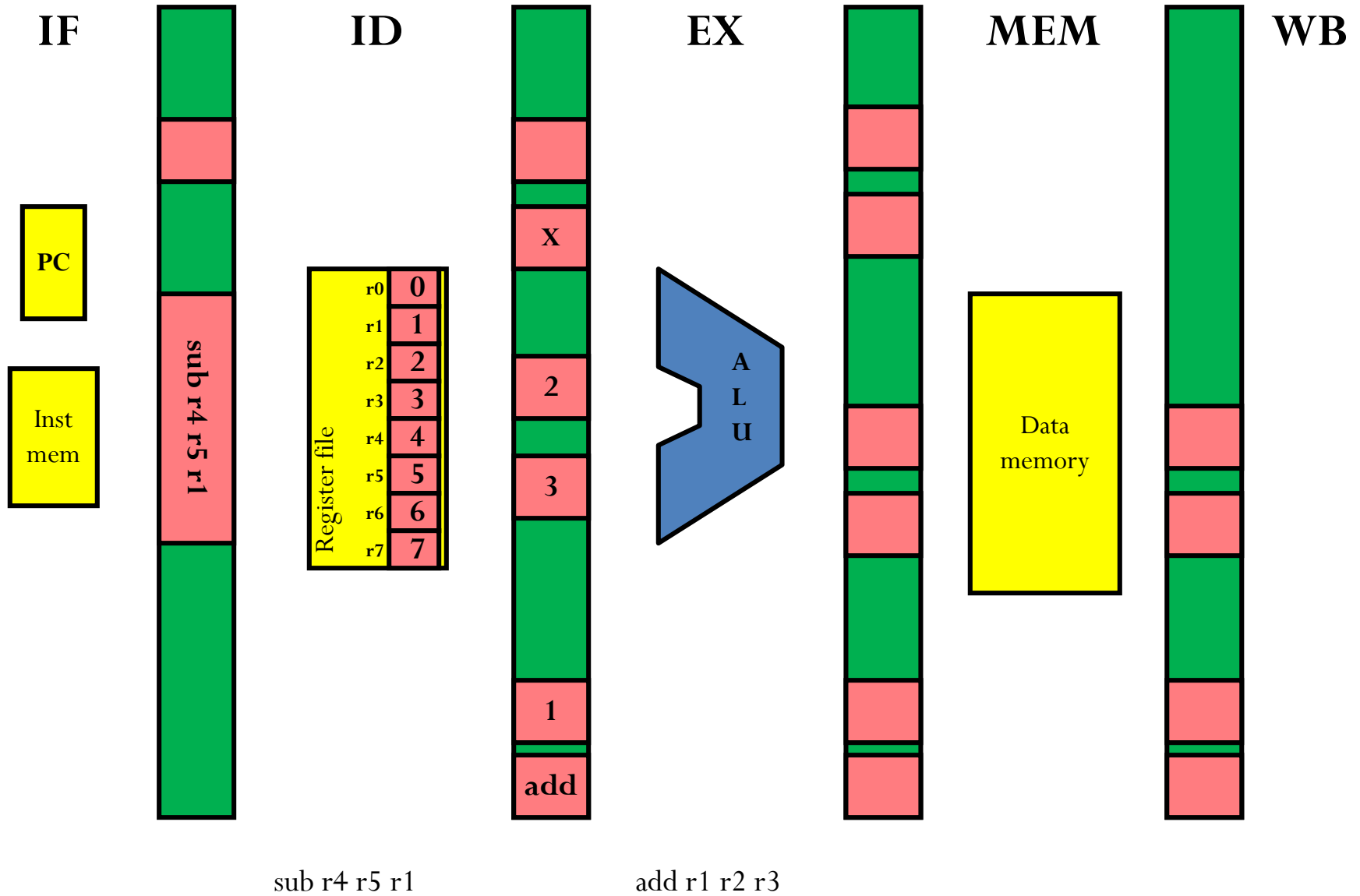

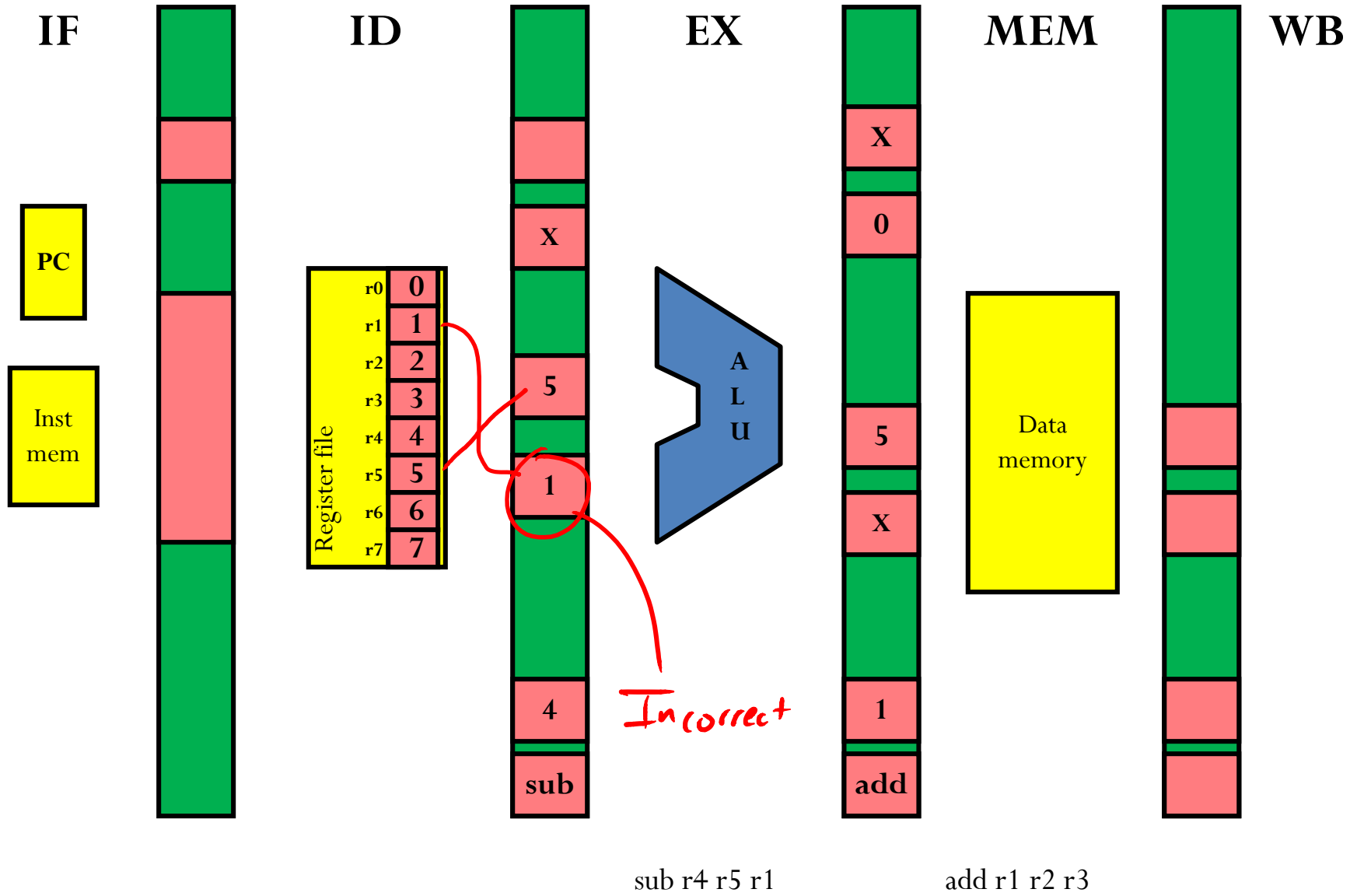


Data Hazards

- **hazard:** A problem in pipeline that leads to inconsistent results.
- **data hazard:** A hazard due to an instruction dependent on data produced by a later instruction in the pipeline.
- First question to ask:
 - How far apart, at a minimum, must dependent instructions be to avoid a data hazard?


Data Hazards

add	r1	r2	r3
sub	r4	r5	r1

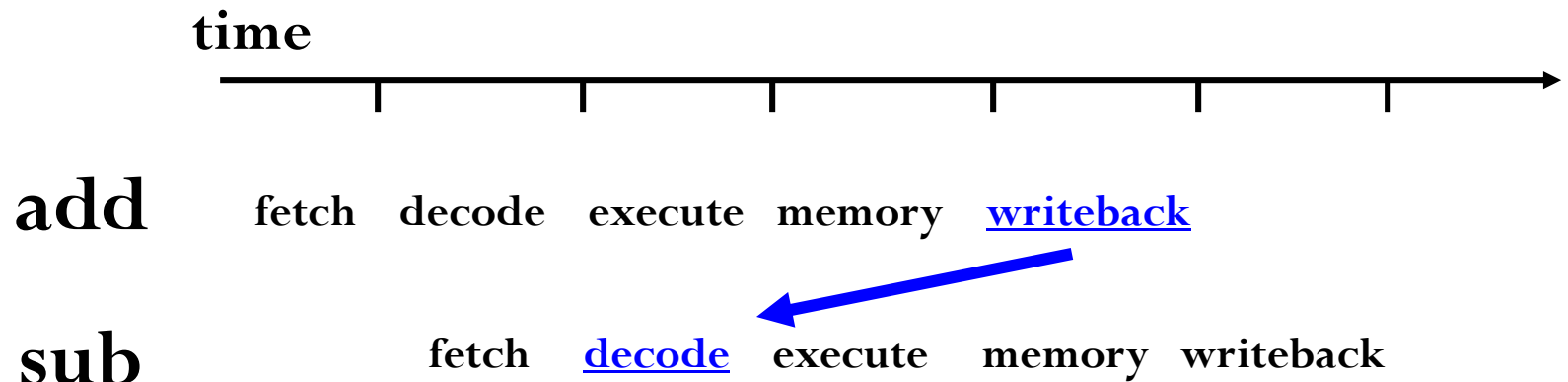

Data Hazards

add	r1	r2	r3	
add	r0	r0	r0	← nop
sub	r4	r5	r1	

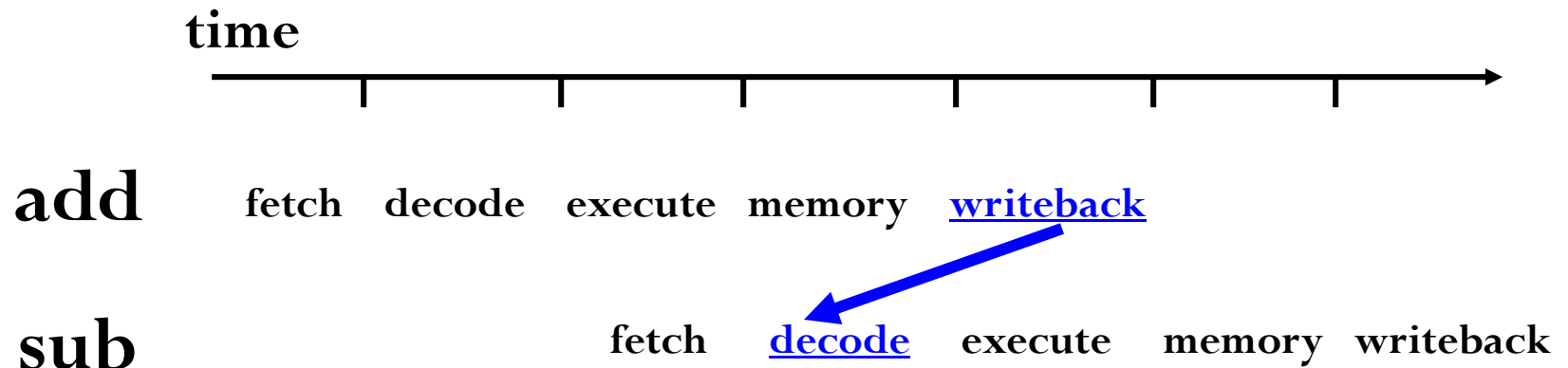

Data Hazards

add	r1	r2	r3
add	r0	r0	r0
add	r0	r0	r0
sub	r4	r5	r1

time



add

fetch decode execute memory writeback

sub

fetch decode execute



Assume that register is written in first half of cycle,
read in second half clock cycle.

Data Hazards in ANNA

- A data hazard occurs in the ANNA pipeline when an instruction is dependent on the result of either of the two instructions that precede it.
- Dependent instructions must be separated with at least two additional instructions to avoid data hazards.
- Are data hazards possible with memory (i.e. a load is dependent on the value of a store)?

No - reads and writes occur in the same stage.
(loads) (stores)

Class Problem

How many data hazards do you see?

SIX

The diagram illustrates six data hazards in the following MIPS assembly code:

```
add r1, r2, r3
and r3, r1, r4
sub r7, r3, r1
lw r7, r3, 7
sw r7, r3, 6
lui r7, 0x56
```

The hazards are identified by colored circles and arrows:

- Red:** `r1` in `add` is used in `and` and `sub`.
- Green:** `r3` in `add` is used in `sub` and `lw`.
- Yellow:** `r3` in `and` is used in `sub` and `lw`.
- Purple:** `r1` in `and` is used in `sub`.
- Dark Green:** `r7` in `sub` is used in `lw` and `sw`.
- Brown:** `r7` in `sw` is used in `lui`.

Handling Data Hazards

- The microprocessor detects if a data hazard occurs. If so, stall the pipeline.
- Detection:
 - Compare the two register sources (if used) with the destination registers (if used) of the previous two instructions sent to EX stage.
- Stall:
 - Keep current instructions in fetch and decode.
 - Pass a nop (`add r0 r0 r0`) to EX stage.

IF

ID

EX

MEM



WB

PC


Inst
mem



Register file	r0	0
	r1	1
	r2	2
	r3	3
	r4	4
	r5	5
	r6	6
	r7	7

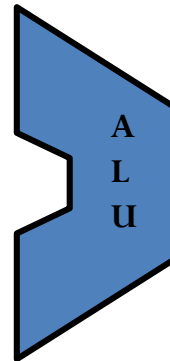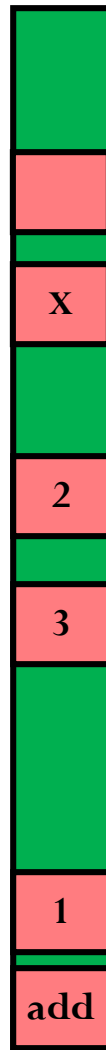

Data
memory

 

not r6 r7

sub r4 r5 r1

add r1 r2 r3

IF

ID

EX

MEM

WB




PC

Inst
mem

Register file	r0	0
	r1	1
	r2	2
	r3	3
	r4	4
	r5	5
	r6	6
	r7	7

A
L
U

Data
memory

 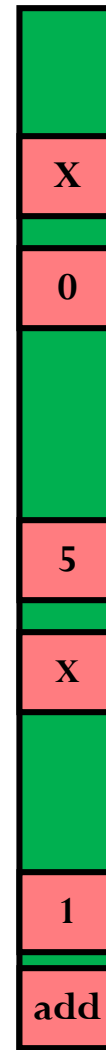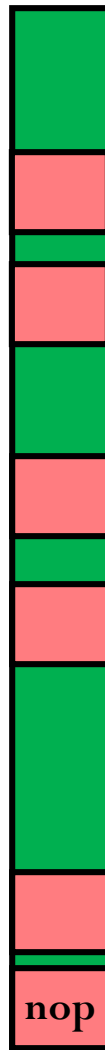

not r6 r7

sub r4 r5 r1

add r0 r0 r0

add r1 r2 r3

IF

ID

EX

MEM

WB




PC

Inst
mem

Register file	r0	0
	r1	5
	r2	2
	r3	3
	r4	4
	r5	5
	r6	6
	r7	7

A
L
U

Data
memory

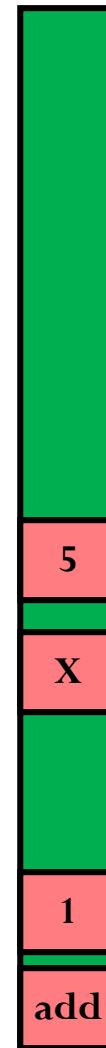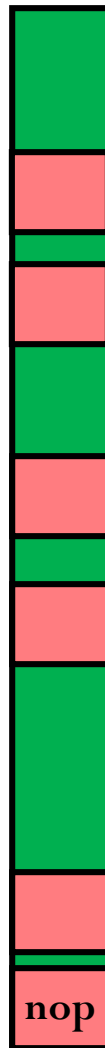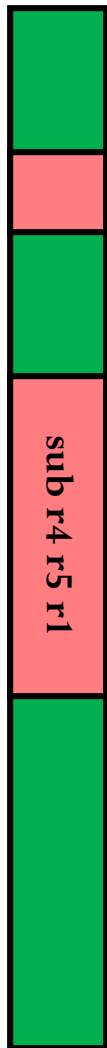

not r6 r7

sub r4 r5 r1

add r0 r0 r0

add r0 r0 r0

add r1 r2 r3

IF

ID

EX

MEM

WB

PC

Inst
mem


Register file	r0	0
	r1	5
	r2	2
	r3	3
	r4	4
	r5	5
	r6	6
	r7	7

A
L
U

Data
memory




not r6 r7

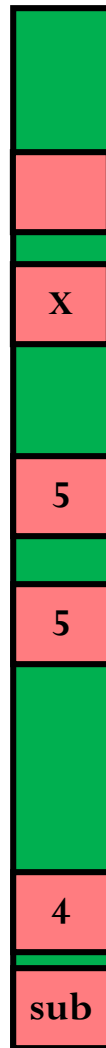

sub r4 r5 r1



add r0 r0 r0

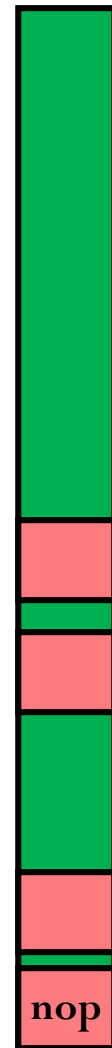

add r0 r0 r0

Time Graph


Time:	1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	16	17	18	19	20
add r1 r2 r3	IF	ID	EX	ME	WB															
and r3 r1 r4		IF	ID	ID	ID	EX	ME	WB												
sub r7 r3 r1			IF	IF	IF	ID	ID	ID	EX	ME	WB									
lw <u>r7</u> r3 -7						IF	IF	IF	ID	EX	ME	WB								
sw <u>r7</u> r3 6									IF	ID	ID	ID	EX	ME	WB					
lui r7 0x56										IF	IF	IF	ID	EX	ME	WB				

$$CPI = \frac{16}{6} = 2.67$$

Branches in Pipelines

Consider a `bez` instruction in pipeline:

```
bez  r1  0x10
sub  r3  r4  r5
```

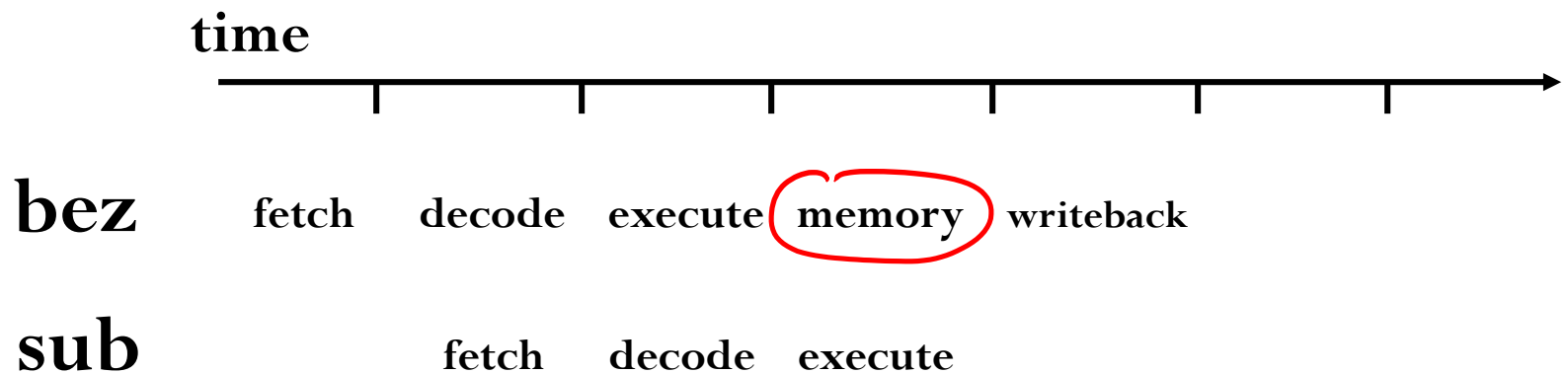

Control Hazards

- A **control hazard** occurs anytime a branch or jump instruction is executed.
- Fetch stage does not know what address to fetch next instruction from.
- In ANNA, branches are resolved in the MEM stage.

jalr

Handling Control Hazards: Stall

- Detect a branch and stall fetch.
- Earliest point that a branch can be detected is decode.
 - Detection is easy: look for branch or jump opcode.
- Stall:
 - Keep current instruction in fetch.
 - Pass nop to decode stage (not execute)!

IF

ID

EX

MEM

WB

30

Inst
mem

bgez r4 0x5

Register file	r0	0
	r1	1
	r2	2
	r3	3
	r4	4
	r5	5
	r6	6
	r7	7




A
L
U

Data
memory

Case 1:
branch is
taken

add r1 r2 r3

bgez r4 0x5

 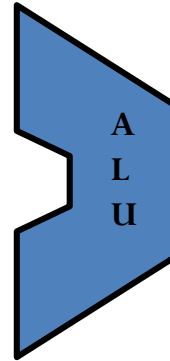 


IF

ID



EX

MEM

WB

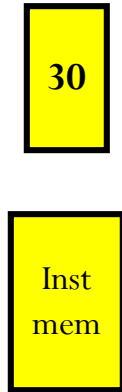

Register file	r0	0
	r1	1
	r2	2
	r3	3
	r4	4
	r5	5
	r6	6
	r7	7

 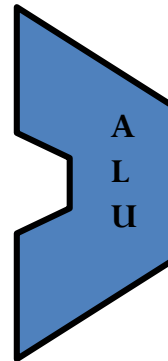

add r1 r2 r3

bgz r4 0x5



IF

ID






EX

MEM

WB

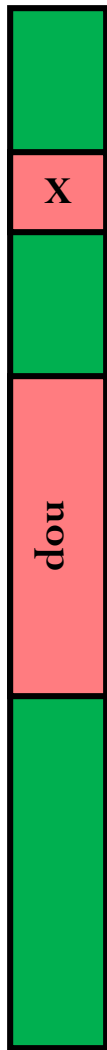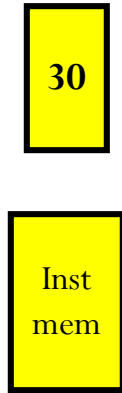

Register file	r0	0
	r1	1
	r2	2
	r3	3
	r4	4
	r5	5
	r6	6
	r7	7

 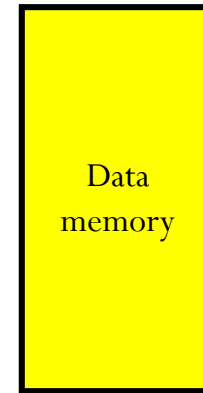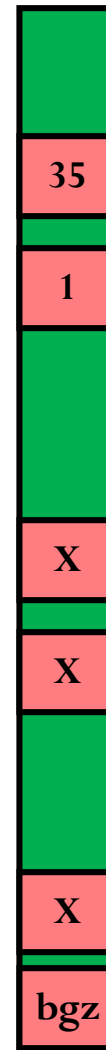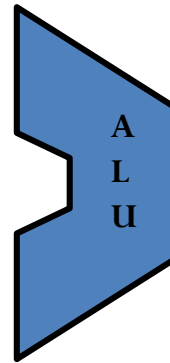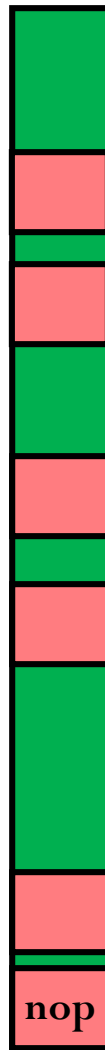

add r1 r2 r3

bgz r4 0x5

IF

ID

EX

MEM

WB

35

Inst
mem

don

Register file

r0	0
r1	1
r2	2
r3	3
r4	4
r5	5
r6	6
r7	7

A
L
U

Data
memory

nop

nop

bgz

sw r5 r8 3

bgz r4 0x5

IF

ID

EX

MEM

WB

30

Inst
mem

30

bez r4 0x5

Register file	r0	0
	r1	1
	r2	2
	r3	3
	r4	4
	r5	5
	r6	6
	r7	7

A
L
U

Data
memory

Case 2:
branch is
not taken

add r1 r2 r3

bez r4 0x5


IF

ID

EX




MEM

WB

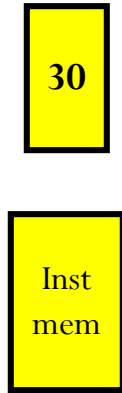

r0	0
r1	1
r2	2
r3	3
r4	4
r5	5
r6	6
r7	7

Register file

 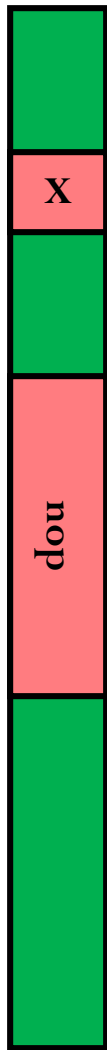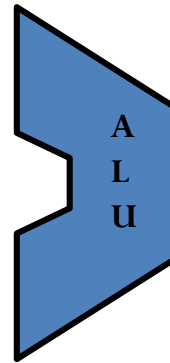

add r1 r2 r3

bez r4 0x5


IF

ID






EX

MEM

WB

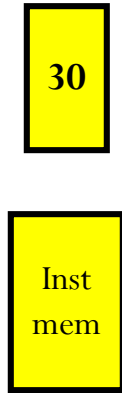

Register file	r0	0
	r1	1
	r2	2
	r3	3
	r4	4
	r5	5
	r6	6
	r7	7

 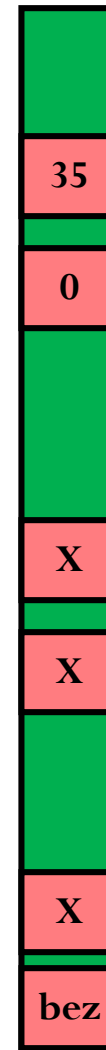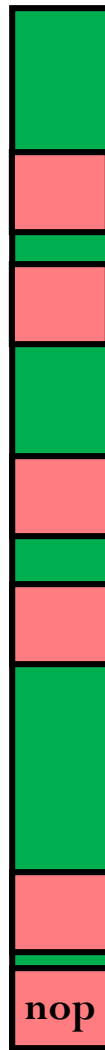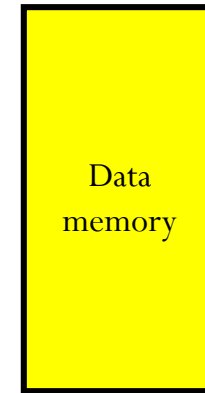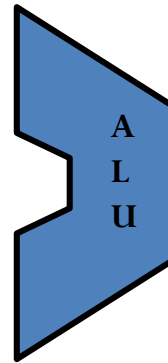

add r1 r2 r3

bez r4 0x5

IF

ID

EX

MEM

WB

30

Inst
mem

don

Register file

r0	0
r1	1
r2	2
r3	3
r4	4
r5	5
r6	6
r7	7

A
L
U

Data
memory

nop

nop

bez

add r1 r2 r3

bez r4 0x5

Pipelining Performance


- CPI (ignore start up)
 - Without hazards: 1
 - With hazards: > 1
- Cycle time:
 - Comparable to multiple cycle implementation
- Overall performance:
 - Better than single cycle or multiple cycle
 - Can be improved with enhancements


Improving Performance Further

- Data forwarding
- Branch prediction
- Reordering instructions
- Parallel pipelines (superscalar)

Data Forwarding


- Observation: The value that will be written to the register is known at the EX stage for arithmetic and logic operations.
- **Data Forwarding:** Find the result of a previous instruction in a future pipeline register and forward it to the EX stage.
- Prevents stalling the pipeline for most (but not all) data hazards.
 - Result for `lw` not known until MEM stage.
- Requires more hardware but is worth it!

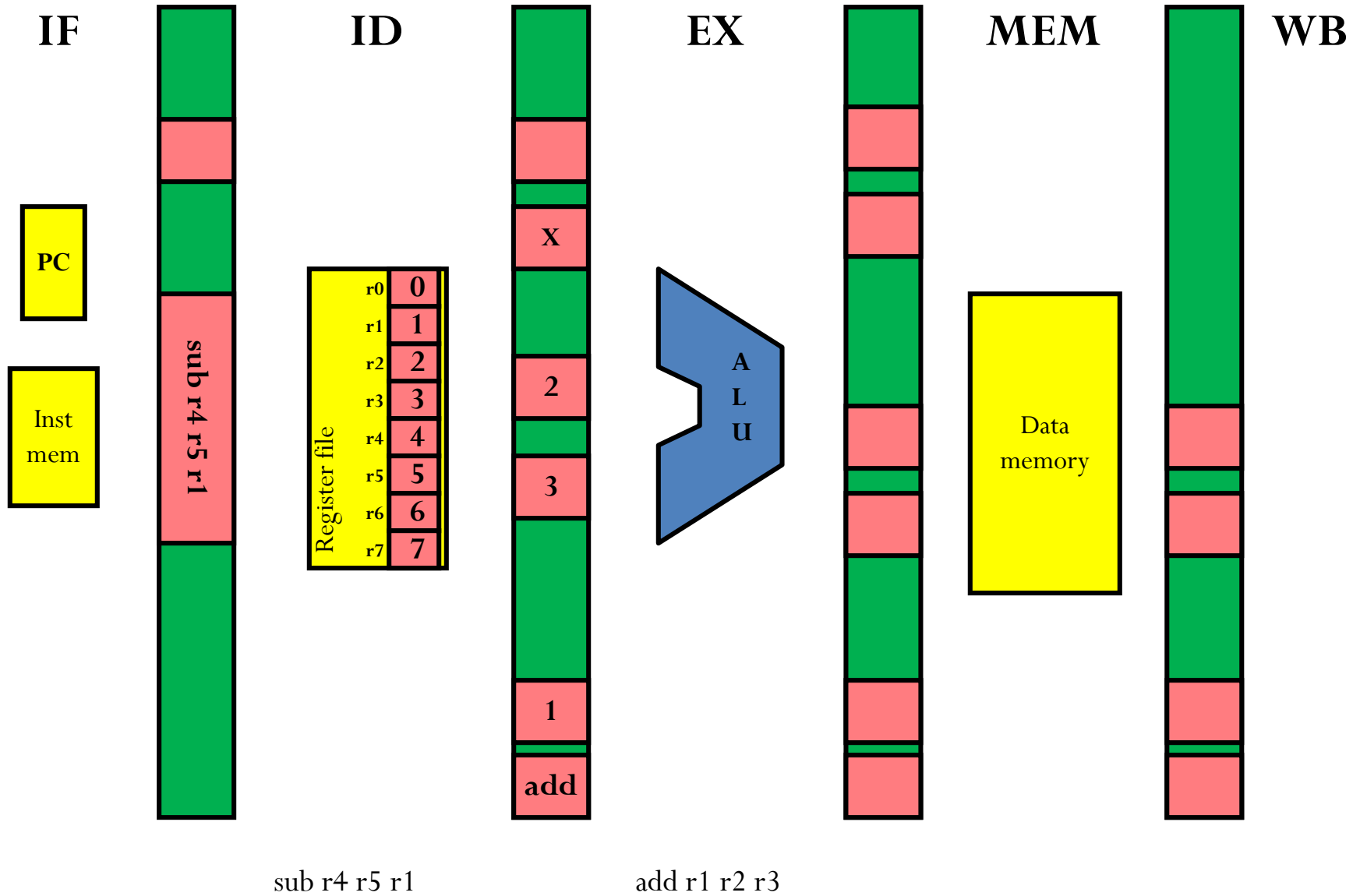

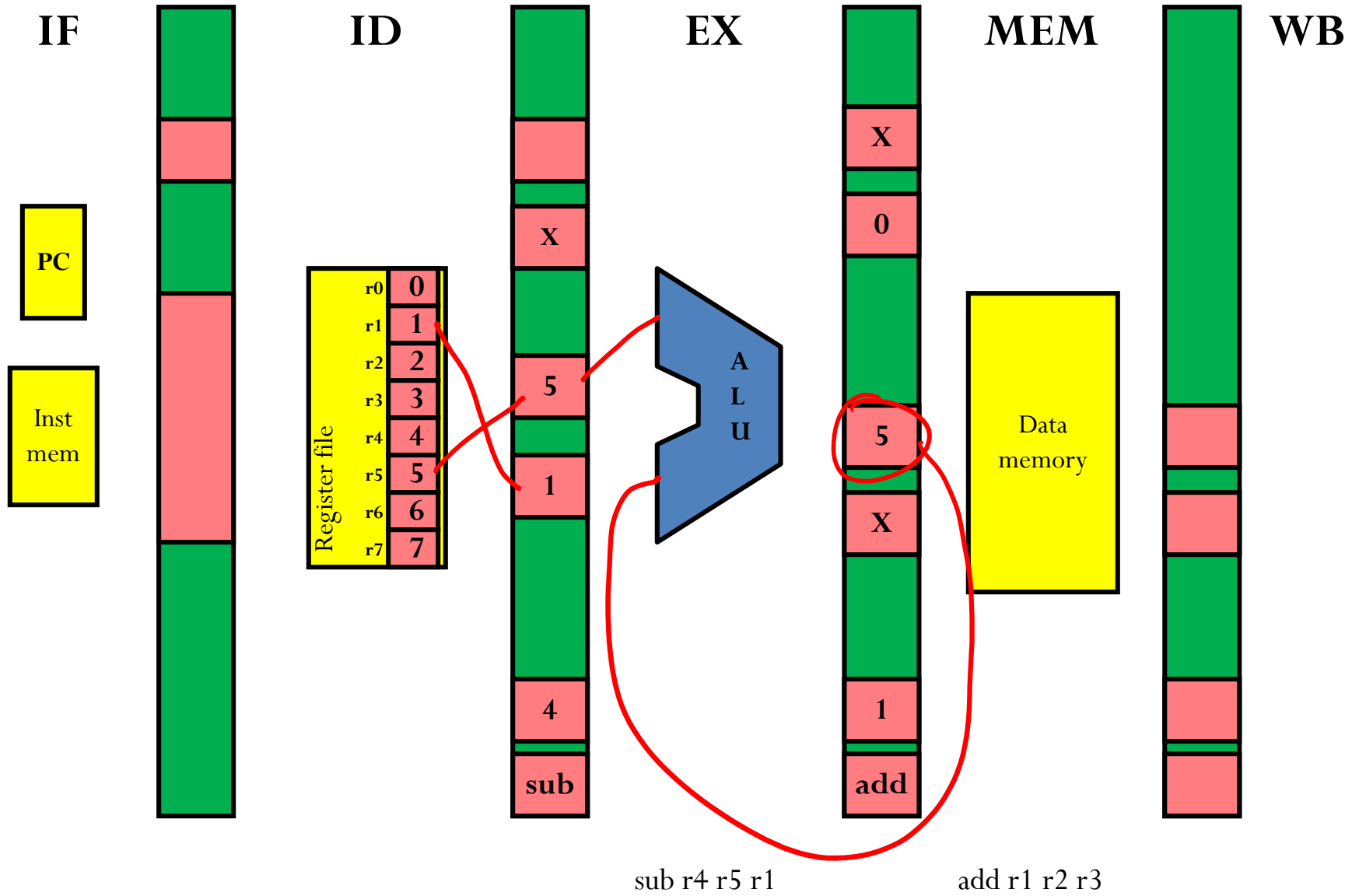

Branch Prediction

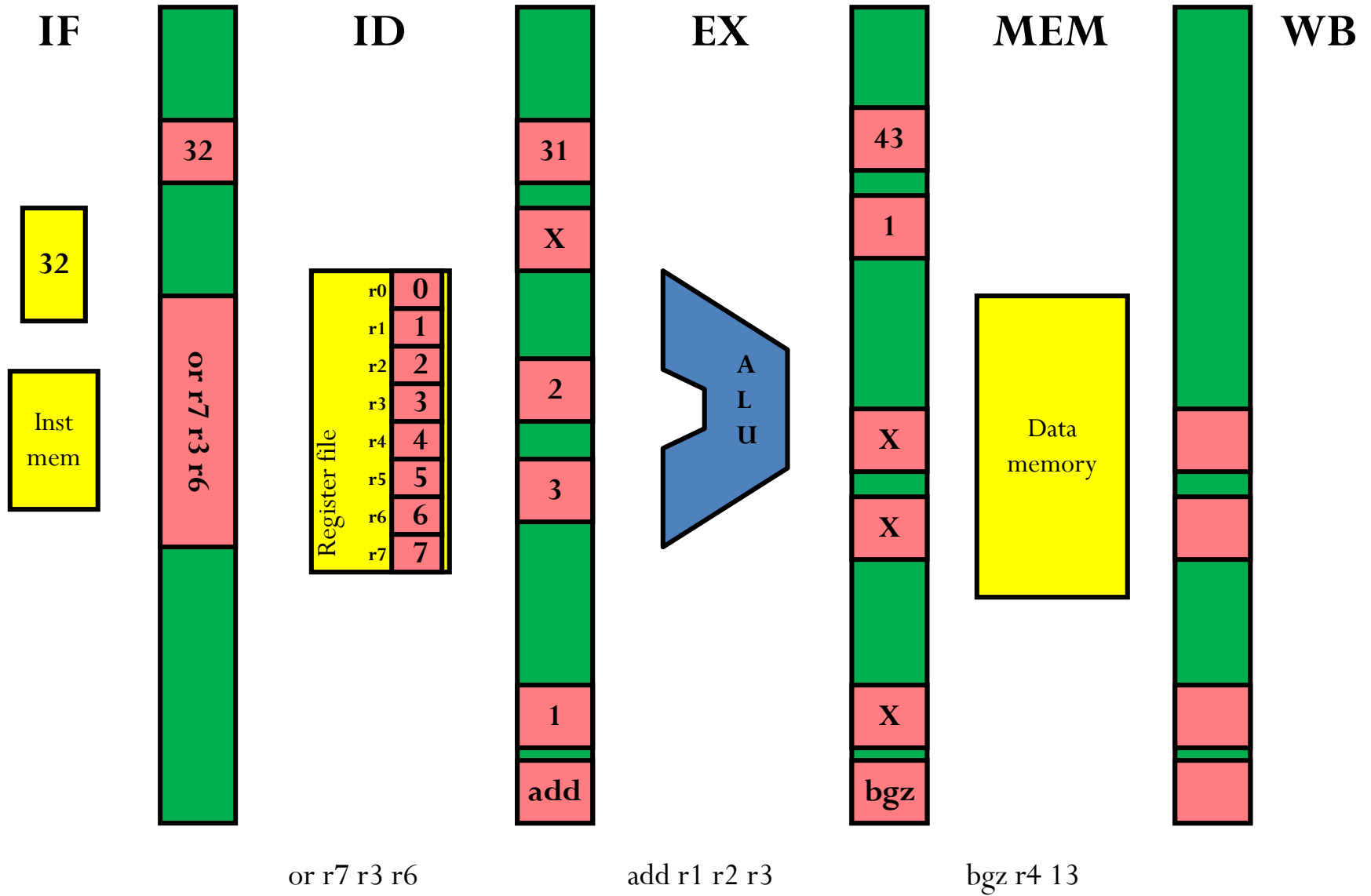- 3 cycle delay is not necessary all the time.
- Simple prediction: assume branch is not taken.
 - Continue to populate pipeline with instructions at PC+1, PC+2, ...
- If branch is not taken → no delay.
- If branch is taken:
 - Squash all instructions in pipeline.
 - Start fetching from target address next cycle.



IF

ID

EX

MEM

WB





43

Inst
mem



r0	0
r1	1
r2	2
r3	3
r4	4
r5	5
r6	6
r7	7

Register file

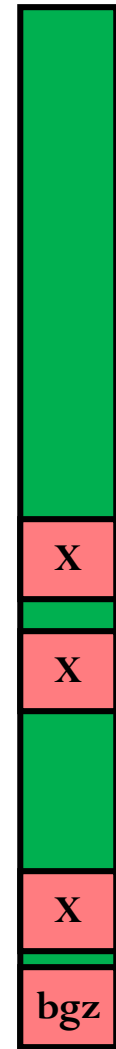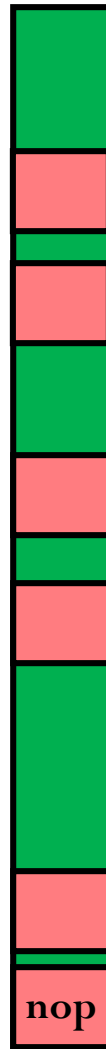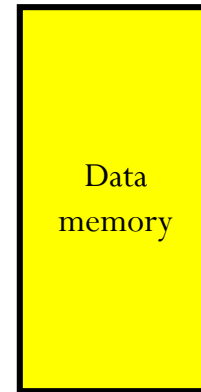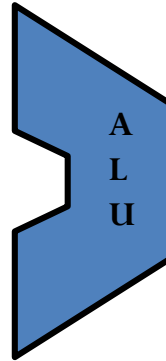

lw r10 r1 r2 r3
r1 r6 3


bgz r4 13

Summarizing Pipelining

- With data forwarding and branch prediction, only stall ANNA in the following cases:
 - A dependent instruction immediately follows a lw (stall for one cycle).
 - A branch is taken (squashes three instructions).
- In real processors:
 - Some instructions may take longer than one cycle (causing stalls) *to execute*
 - Examples: multiply, divide, floating point arithmetic
 - Additional stalls due to cache misses.
 - Need to deal with I/O.

Pipelining as a Computing Concept

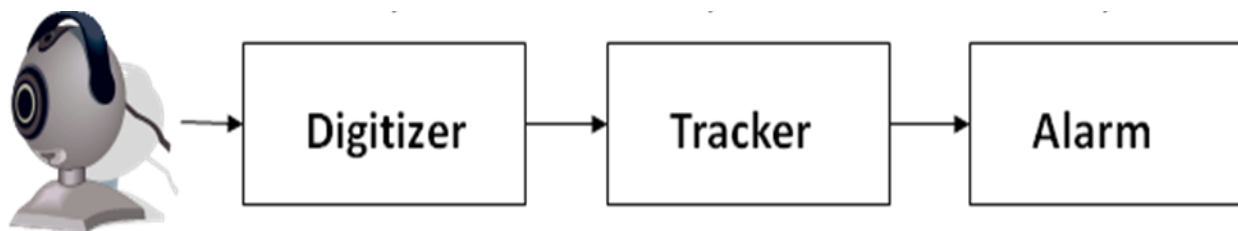- Pipelining is not limited to microprocessors.
- Pipelining can be applied to computing systems.
 - Useful in cases where a calculation is broken into phases.
 - Form of parallelism.
- Example: Real-time surveillance camera:



Outline

- Introduction to Microarchitecture
- ANNA Datapath
- ANNA Control
- Performance
- Pipelining
- **Additional Performance Optimizations**

Better Branch Prediction

- Can do more sophisticated predictions:
 - Predict taken ($\sim 60\%$ branches are taken)
 - Predict the same as last time
 - Predict based on pattern (loops)
- Modern branch predictors are correct over 90% of the time.


Reordering Instructions

- In order to avoid data hazards, it may be possible to reorder instructions.
- Goals:
 - Move dependent instructions further away.
 - Cannot violate program functionality.
- Especially helpful for slow instructions:
 - loads / store (if not in cache)
 - multiply / divide / FP operations
- Reordering can be done by the compiler or inside the CPU.

Parallel Pipelines (Superscalar)

- If you max out the performance of the pipeline and still want more, what can you do?
 - Build a second pipeline
- Two or more instructions can be executed at the same time.
 - Must be independent.
- It is possible to forward data between the two pipelines.
- Lower level parallelism than multiple cores.

Intel Core Microarchitecture

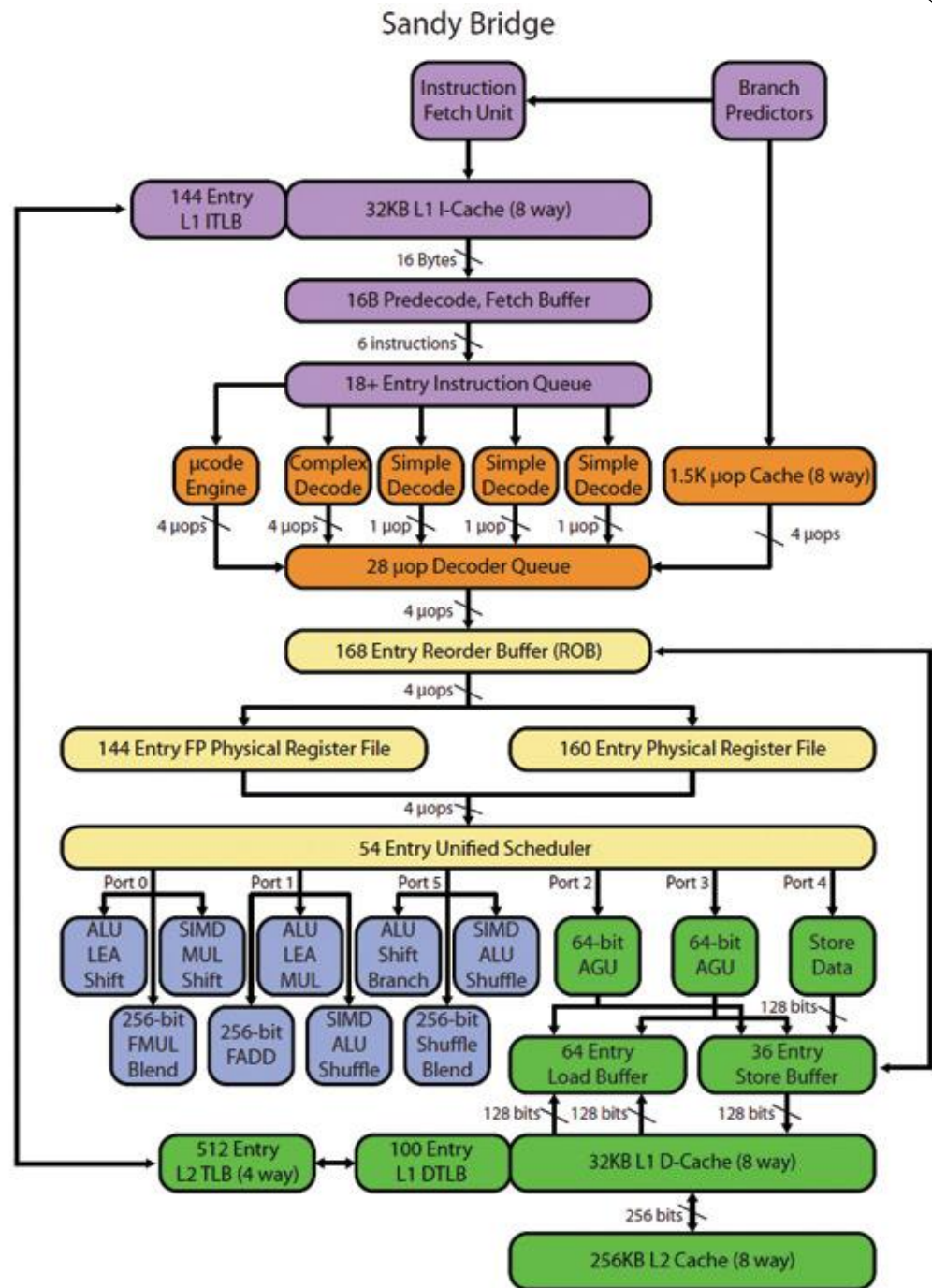

Thank You!