

## CPSC 2500


### Computer Organization

#### Homework 3 (100 points)

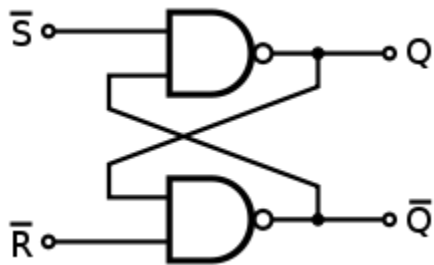**Due: Oct 30, 9:20 AM (in class)**

**NOTE:** Please write/print your answers to the following questions and submit it in class on Oct 30 (Friday). Please **DO NOT** submit on Canvas or via email. This assignment is to be done individually; you can discuss the questions with your classmates, but you should write your answers independently.


**1A.** For the circuit shown below, complete the truth table. (10)



$\overline{S}$	$\overline{R}$	$Q_{\text{curr}}$	$Q_{\text{new}}$
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

**1B.** How does the operation of the circuit in 1A compare to the operation of SR latch we discussed in class? (10)

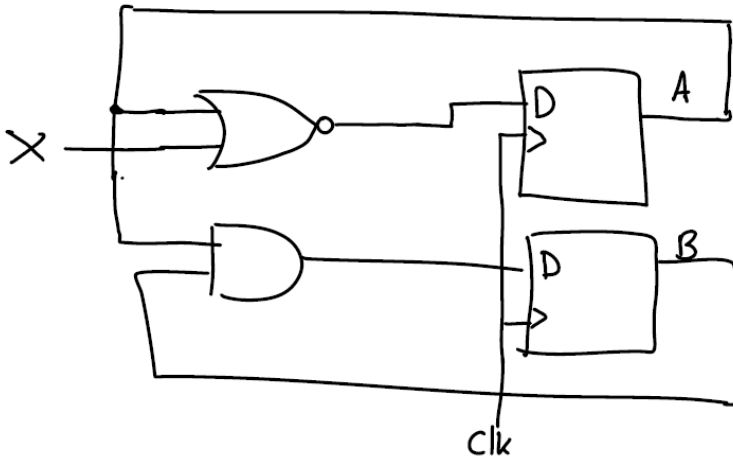**2.** Complete the truth table for the following sequential circuit. (10)



Current State		Input	Next State	
A	B	X	A	B
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

**3.** Using logic gates, draw a circuit diagram for comparing two 32-bit numbers. The circuit should return 1 if the numbers match, else return 0. Use the shorthand notation for multiple-bit line when drawing the circuit. (10)

#### 4. Memory Organization

- A. For a byte-addressable memory, how many address bits are needed for 256 MB? (10)
- B. For a byte-addressable memory, how much memory can be accessed using a 34 bit address? Express your answer using metric prefixes. (10)
- C. For a word-addressable memory where each word is 64 bits, how much memory can be accessed using a 34 bit address? Express your answer using metric prefixes. (10)
- D. For a word-addressable memory where each word is 64 bits, how many address bits are needed for 256 MB? (10)

#### 5. Multiplexers

In this question, we are going to use the 8 input multiplexer shown in figure below to implement an even parity function, i.e., the output of the function is 1 if and only if an even number of inputs are 1. Assume that you have three input variables: A, B, C. (Note: zero is an even number.)

- A. Create a truth table for the three variable even parity function. (10)
- B. **Using the following 8-input multiplexer**, implement the Boolean function for which you created the truth table in part A. (10)

